
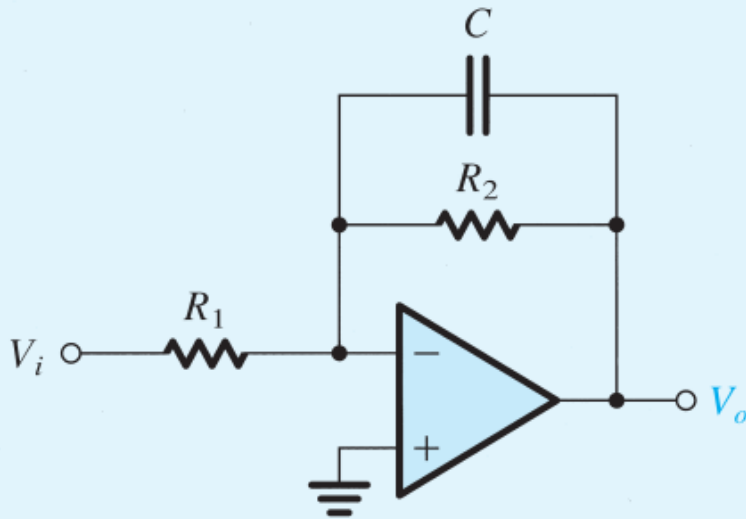


**D 2.86** Figure P2.86 shows a circuit that performs a low-pass STC function. Such a circuit is known as a first-order, low-pass active filter. Derive the transfer function and show that the dc gain is  $(-R_2/R_1)$  and the 3-dB frequency  $\omega_0 = 1/CR_2$ . Design the circuit to obtain an input resistance of 10 k $\Omega$ , a dc gain of 40 dB, and a 3-dB frequency of 1 kHz. At what frequency does the magnitude of the transfer function reduce to unity?

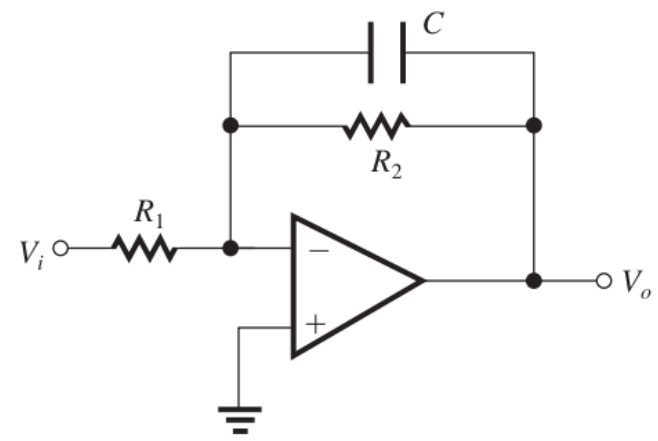

**Figure P2.86**



$$\text{Let } Z_2 = R_2 \parallel \frac{1}{sC} \text{ and } Z_1 = R_1$$

$$\begin{aligned} \frac{V_o}{V_i} &= -\frac{Z_2}{Z_1} = -\frac{Y_1}{Y_2} = -\frac{1/R_1}{\frac{1}{R_2} + sC} \\ &= -\frac{(R_2/R_1)}{1 + sCR_2} \end{aligned}$$


This function is of the STC low-pass type, having a dc gain of  $-\frac{R_2}{R_1}$  and a 3-dB frequency

$$\omega_0 = \frac{1}{CR_2}$$

$$R_{\text{in}} = R_1 = 10 \text{ k}\Omega$$

$$\text{dc gain} = 40 \text{ dB} = 100$$
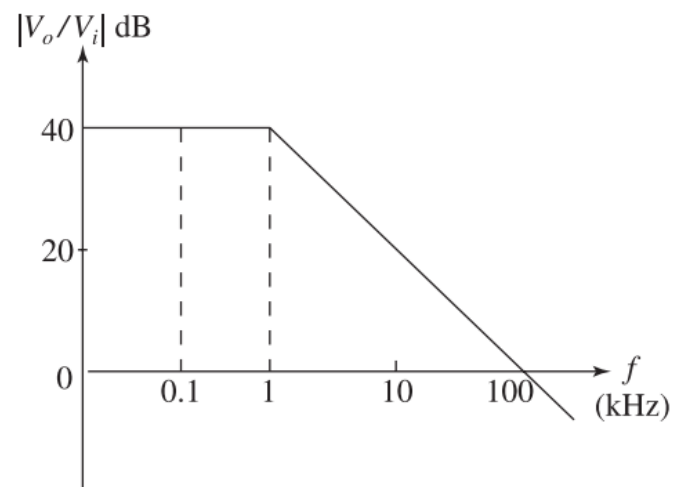
$$\therefore 100 = \frac{R_2}{R_1} \Rightarrow R_2 = 100R_1 = 1 \text{ M}\Omega$$



3-dB frequency at 1 kHz

$$\therefore \omega_0 = 2\pi \times 1 \times 10^3 = \frac{1}{CR_2}$$

$$C = \frac{1}{2\pi \times 1 \times 10^3 \times 10^6} = 0.16 \text{ nF}$$

From the Bode plot shown in previous column, the unity-gain frequency is 100 kHz.

**D 2.92** Figure P2.92 shows a circuit that performs the high-pass, single-time-constant function. Such a circuit is known as a first-order high-pass active filter. Derive the transfer function and show that the high-frequency gain is  $(-R_2/R_1)$  and the 3-dB frequency  $\omega_0 = 1/CR_1$ . Design the circuit to obtain a high-frequency input resistance of 1 k $\Omega$ , a high-frequency gain of 40 dB, and a 3-dB frequency of 2 kHz. At what frequency does the magnitude of the transfer function reduce to unity?


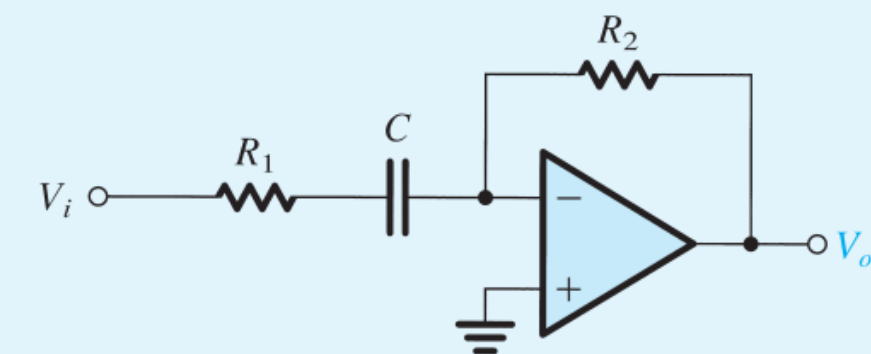


Figure P2.92

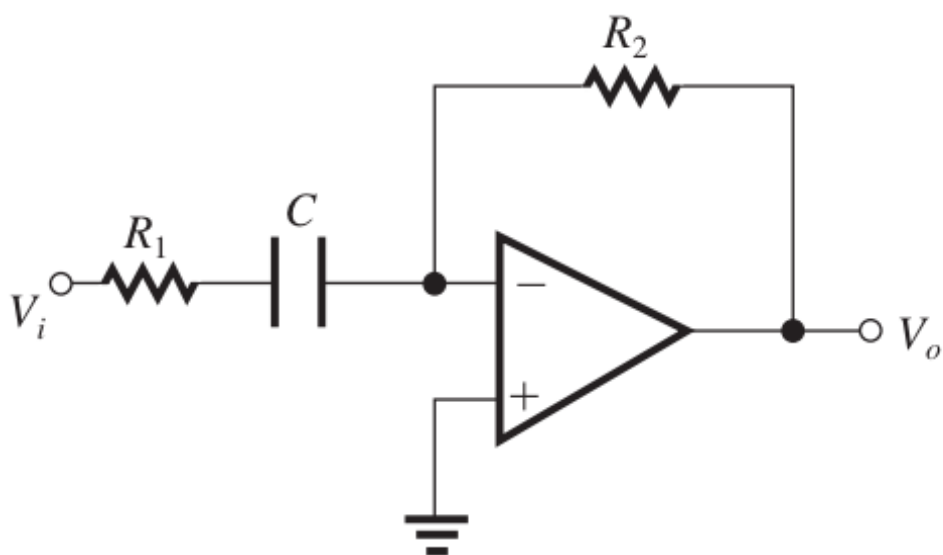

$$\frac{V_o}{V_i} = -\frac{Z_2}{Z_1} = -\frac{R_2}{R_1 + \frac{1}{sC}}$$

Thus,

$$\frac{V_o}{V_i} = -\frac{(R_2/R_1)s}{s + \frac{1}{CR_1}}$$

which is that of an STC high-pass type.

$$\text{High-frequency gain } (s \rightarrow \infty) = -\frac{R_2}{R_1}$$

$$\text{3-dB frequency } (\omega_{3\text{dB}}) = \frac{1}{CR_1}$$

For a high-frequency input resistance of 1 k $\Omega$ , we select  $R_1 = 1 \text{ k}\Omega$ . For a high-frequency gain of 40 dB,

$$\frac{R_2}{R_1} = 100 \Rightarrow R_2 = 100 \text{ k}\Omega$$


For  $f_{3\text{dB}} = 2 \text{ kHz}$ ,

$$\frac{1}{2\pi CR_1} = 2 \times 10^3$$

$$\Rightarrow C = 79 \text{ nF}$$

The magnitude of the transfer function reduces from 40 dB to unity (0 dB) in two decades. Thus
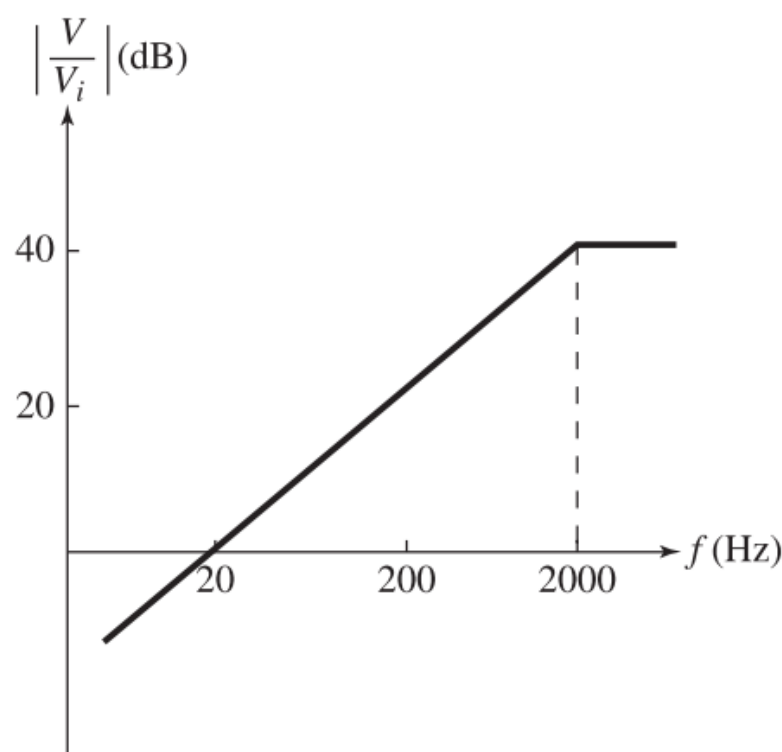
$$f \text{ (unity gain)} = \frac{f_{3\text{dB}}}{100} = \frac{2000}{100} = 20 \text{ Hz}$$



**D \*2.117** This problem illustrates the use of cascaded closed-loop amplifiers to obtain an overall bandwidth greater than can be achieved using a single-stage amplifier with the same overall gain.

- (a) Show that cascading two identical amplifier stages, each having a low-pass STC frequency response with a 3-dB frequency  $f_1$ , results in an overall amplifier with a 3-dB frequency given by

$$f_{3\text{dB}} = \sqrt{\sqrt{2}-1} f_1$$

- (b) It is required to design a noninverting amplifier with a dc gain of 40 dB utilizing a single internally compensated op amp with  $f_t = 2$  MHz. What is the 3-dB frequency obtained?
- (c) Redesign the amplifier of (b) by cascading two identical noninverting amplifiers each with a dc gain of 20 dB. What is the 3-dB frequency of the overall amplifier? Compare this to the value obtained in (b) above.

$$1 + \left( \frac{f_{3\text{dB}}}{f_1} \right)^2 = \sqrt{2}$$

$$f_{3\text{dB}} = f_1 \sqrt{\sqrt{2}-1} \quad \text{Q.E.D.}$$

$$(b) \quad 40 \text{ dB} = 20 \log G_0 \Rightarrow G_0 = 100 = 1 + \frac{R_2}{R_1}$$

$$f_{3\text{dB}} = \frac{f_t}{1 + \frac{R_2}{R_1}} = \frac{2 \text{ MHz}}{100} = 20 \text{ kHz}$$

$$\therefore GB = 1 \cdot f_t = G \cdot f$$

- (c) Each stage should have 20-dB gain or  $1 + \frac{R_2}{R_1} = 10$  and therefore a 3-dB frequency of

$$f_1 = \frac{2 \times 10^6}{10} = 2 \times 10^5 \text{ Hz}$$

$$\begin{aligned} \text{The overall } f_{3\text{dB}} &= 2 \times 10^5 \sqrt{\sqrt{2}-1} \\ &= 128.7 \text{ kHz,} \end{aligned}$$

which is 6.4 times greater than the bandwidth achieved using a single op amp, as in case (b) above.

**2.108** (a) Assume two identical stages, each with a gain function:

$$G = \frac{G_0}{1 + j \frac{\omega}{\omega_1}} = \frac{G_0}{1 + j \frac{f}{f_1}}$$

$$G = \frac{G_0}{\sqrt{1 + \left( \frac{f}{f_1} \right)^2}}$$

$$\text{overall gain of the cascade is } \frac{G_0^2}{1 + \left( \frac{f}{f_1} \right)^2}$$

The gain will drop by 3 dB when

**2.126** For an amplifier having a slew rate of  $40 \text{ V}/\mu\text{s}$ , what is the highest frequency at which a 20-V peak-to-peak sine wave can be produced at the output?

**2.114** Slope of the triangle wave  $= \frac{10 \text{ V}}{T/2} = \text{SR}$

Thus  $\frac{10}{T} \times 2 = 20 \text{ V}/\mu\text{s}$


$\Rightarrow T = 1 \mu\text{s}$  or  $f = \frac{1}{T} = 1 \text{ MHz}$

For a sine wave  $v_o = \hat{V}_o \sin(2\pi \times 1 \times 10^6 t)$

$\left. \frac{dv_o}{dt} \right|_{\max} = 2\pi \times 1 \times 10^6 \hat{V}_o = \text{SR}$

$\Rightarrow \hat{V}_o = \frac{20 \times 10^6}{2\pi \times 10^6 \times 1} = 3.18 \text{ V}$

**11.2** Consider the op-amp circuit shown in Fig. P11.2, where the op amp has infinite input resistance and zero output resistance but finite open-loop gain  $A$ .

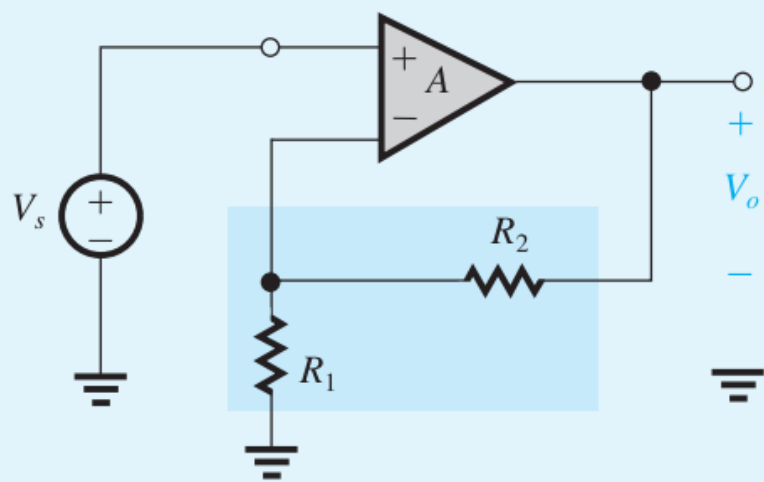

**Figure P11.2**

- (a) Convince yourself that  $\beta = R_1/(R_1 + R_2)$ .  
 (b) If  $R_1 = 10 \text{ k}\Omega$ , find  $R_2$  that results in  $A_f = 10 \text{ V/V}$  for the following three cases: (i)  $A = 1000 \text{ V/V}$ ; (ii)  $A = 200 \text{ V/V}$ ; (iii)  $A = 15 \text{ V/V}$ .  
 (c) For each of the three cases in (b), find the percentage change in  $A_f$  that results when  $A$  decreases by 20%. Comment on the results.

**10.2** (a) Because of the infinite input resistance of the op amp, the fraction of the output voltage  $V_o$  that is fed back and subtracted from  $V_s$  is determined by the voltage divider  $(R_1, R_2)$ , thus

$$\beta = \frac{R_1}{R_1 + R_2}$$

(b) (i)  $A = 1000 \text{ V/V}$

$$A_f = \frac{A}{1 + A\beta}$$

$$10 = \frac{1000}{1 + 1000\beta}$$

$$\Rightarrow \beta = 0.099 \text{ V/V}$$

$$\frac{R_1}{R_1 + R_2} = 0.099$$

$$1 + \frac{R_2}{R_1} = \frac{1}{0.099}$$

$$R_2 = R_1 \left( \frac{1}{0.099} - 1 \right)$$

$$= 10 \left( \frac{1}{0.099} - 1 \right) = 91 \text{ k}\Omega$$

(ii)  $A = 200 \text{ V/V}$

$$10 = \frac{200}{1 + 200\beta}$$

$$\Rightarrow \beta = 0.095 \text{ V/V}$$

$$R_2 = R_1 \left( \frac{1}{0.095} - 1 \right)$$

$$= 10 \left( \frac{1}{0.095} - 1 \right) = 95.3 \text{ k}\Omega$$

(iii)  $A = 15 \text{ V/V}$

$$10 = \frac{15}{1 + 15\beta}$$

$$\Rightarrow \beta = 0.033 \text{ V/V}$$

$$R_2 = 10 \left( \frac{1}{0.033} - 1 \right)$$

$$= 290 \text{ k}\Omega$$

(c) (i)  $A = 1000(1 - 0.2) = 800 \text{ V/V}$

$$A_f = \frac{800}{1 + 800 \times 0.099}$$

$$= 9.975 \text{ V/V}$$

Thus,  $A_f$  changes by

$$= \frac{9.975 - 10}{10} \times 100 = -0.25\%$$

(ii)  $A = 200(1 - 0.2) = 160 \text{ V/V}$

$$A_f = \frac{160}{1 + 160 \times 0.095} = 9.877 \text{ V/V}$$

Thus,  $A_f$  changes by

$$= \frac{9.877 - 10}{10} \times 100 = -1.23\%$$

(iii)  $A = 15(1 - 0.2) = 12 \text{ V/V}$

$$A_f = \frac{12}{1 + 12 \times 0.033} = 8.574$$

Thus,  $A_f$  changes by

$$= \frac{8.575 - 10}{10} \times 100 = -14.3\%$$

We conclude that as  $A$  becomes smaller and hence the amount of feedback  $(1 + A\beta)$  is lower, the desensitivity of the feedback amplifier to changes in  $A$  decreases. In other words, the negative feedback becomes less effective as  $(1 + A\beta)$  decreases.

**11.18** Consider an amplifier having a midband gain  $A_M$  and a low-frequency response characterized by a pole at  $s = -\omega_L$  and a zero at  $s = 0$ . Let the amplifier be connected in a negative-feedback loop with a feedback factor  $\beta$ . Find an expression for the midband gain and the lower 3-dB frequency of the closed-loop amplifier. By what factor have both changed?

$$\mathbf{10.16} \quad A = A_M \frac{s}{s + \omega_L}$$

$$A_f = \frac{A}{1 + A\beta}$$

$$= \frac{A_M s / (s + \omega_L)}{1 + A_M \beta s / (s + \omega_L)}$$

$$= \frac{A_M s}{s + \omega_L + s A_M \beta}$$

$$= \frac{A_M s}{s(1 + A_M \beta) + \omega_L}$$

$$= \frac{A_M}{1 + A_M \beta} \frac{s}{s + \omega_L / (1 + A_M \beta)}$$

Thus,


$$A_{Mf} = \frac{A_M}{1 + A_M \beta}$$

$$\omega_{Lf} = \frac{\omega_L}{1 + A_M \beta}$$

Thus, both the midband gain and the 3-dB frequency are lowered by the amount of feedback,  $(1 + A_M \beta)$ .




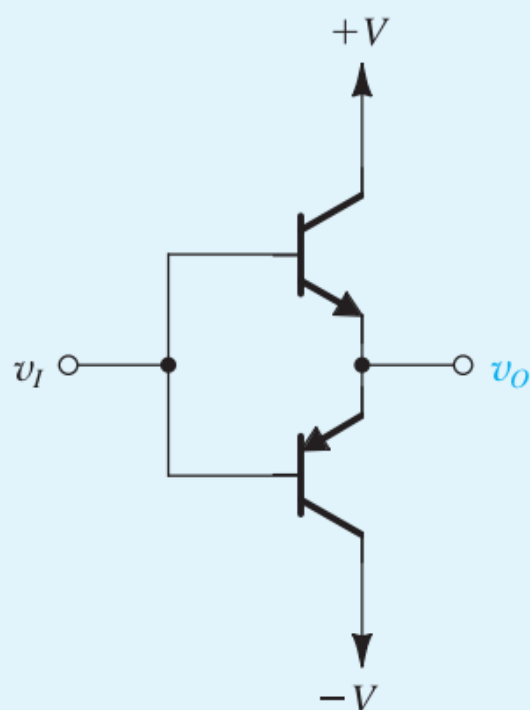**\*11.24** The complementary BJT follower shown in Fig. P11.24(a) has the approximate transfer characteristic shown in Fig. P11.24(b). Observe that for  $-0.7 \text{ V} \leq v_I \leq +0.7 \text{ V}$ , the output is zero. This “dead band” leads to crossover distortion (see Section 12.3). Consider this follower to be driven by the output of a differential amplifier of gain 100



(a)

Figure P11.24

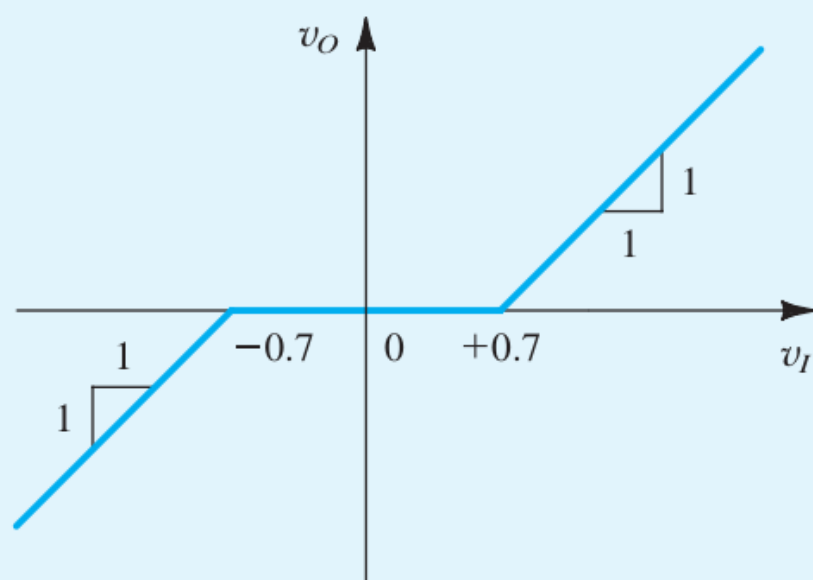

(b)

Figure P11.24 continued

whose positive-input terminal is connected to the input signal source  $v_s$  and whose negative-input terminal is connected to the emitters of the follower. Sketch the transfer characteristic  $v_o$  versus  $v_s$  of the resulting feedback amplifier. What are the limits of the dead band, and what are the gains outside the dead band?

## 10.22

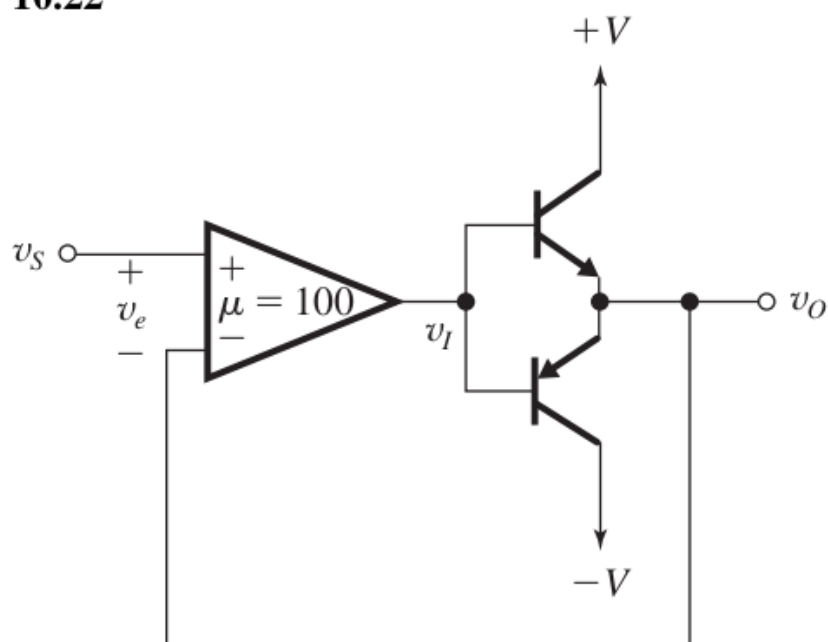


Figure 1

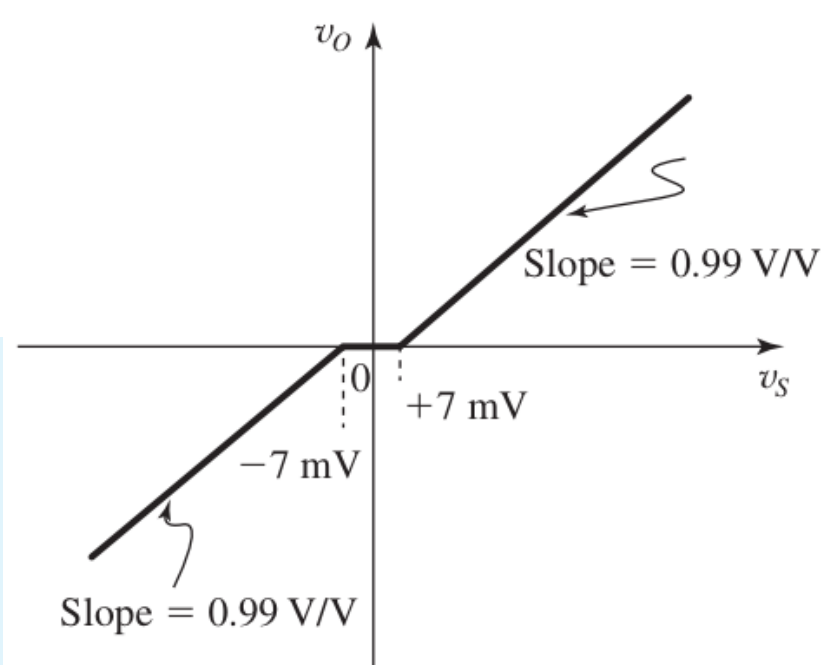


Figure 2

Refer to Fig. 1. For  $v_I = +0.7 \text{ V}$ , we have  $v_O = 0$  and

$$v_e = \frac{v_I}{\mu} = \frac{+0.7}{100} = +7 \text{ mV}$$

Similarly, for  $v_I = -0.7 \text{ V}$ , we obtain  $v_O = 0$  and

$$v_e = \frac{v_I}{\mu} = \frac{-0.7}{100} = -7 \text{ mV}$$


Thus, the limits of the deadband are now  $\pm 7 \text{ mV}$ . Outside the deadband, the gain of the feedback amplifier, that is,  $v_o/v_s$ , can be determined by noting that the open-loop gain  $A \equiv v_O/v_e = 100 \text{ V/V}$  and the feedback factor  $\beta = 1$ , thus

$$\begin{aligned} A_f &\equiv \frac{v_o}{v_s} = \frac{A}{1 + A\beta} \\ &= \frac{100}{1 + 100 \times 1} = 0.99 \text{ V/V} \end{aligned}$$

The transfer characteristic is depicted in Fig. 2.

**D 11.31** Figure P11.31 shows a series–shunt feedback amplifier known as a “feedback triple.” All three MOSFETs are biased to operate at  $g_m = 4 \text{ mA/V}$ . You may neglect their  $r_o$ ’s.

- (a) Select a value for  $R_F$  that results in a closed-loop gain that is ideally 10 V/V.

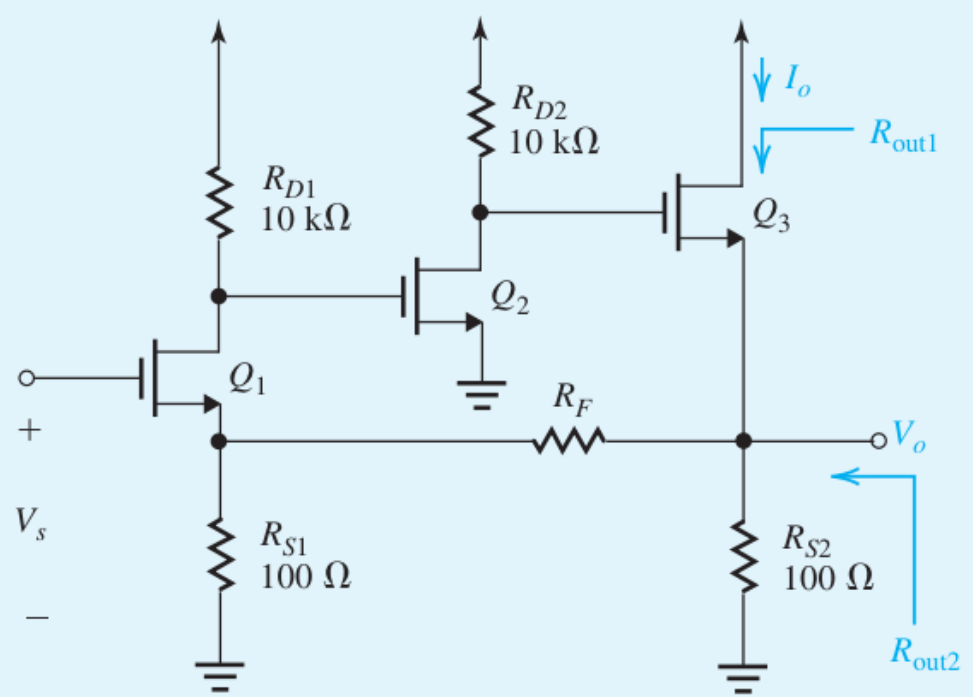

**Figure P11.31**

- (b) Determine the loop gain  $A\beta$  and hence the value of  $A_f$ . By what percentage does  $A_f$  differ from the ideal value you designed for? How can you adjust the circuit to make  $A_f$  equal to 10?

**10.28** (a) The feedback network consists of the voltage divider  $(R_F, R_{S1})$ . Thus,

$$\beta = \frac{R_{S1}}{R_{S1} + R_F}$$


and the ideal value of the closed-loop gain is

$$A_f = \frac{1}{\beta} = 1 + \frac{R_F}{R_{S1}}$$

$$10 = 1 + \frac{R_F}{0.1}$$

$$\Rightarrow R_F = 0.9 \text{ k}\Omega$$

(b)

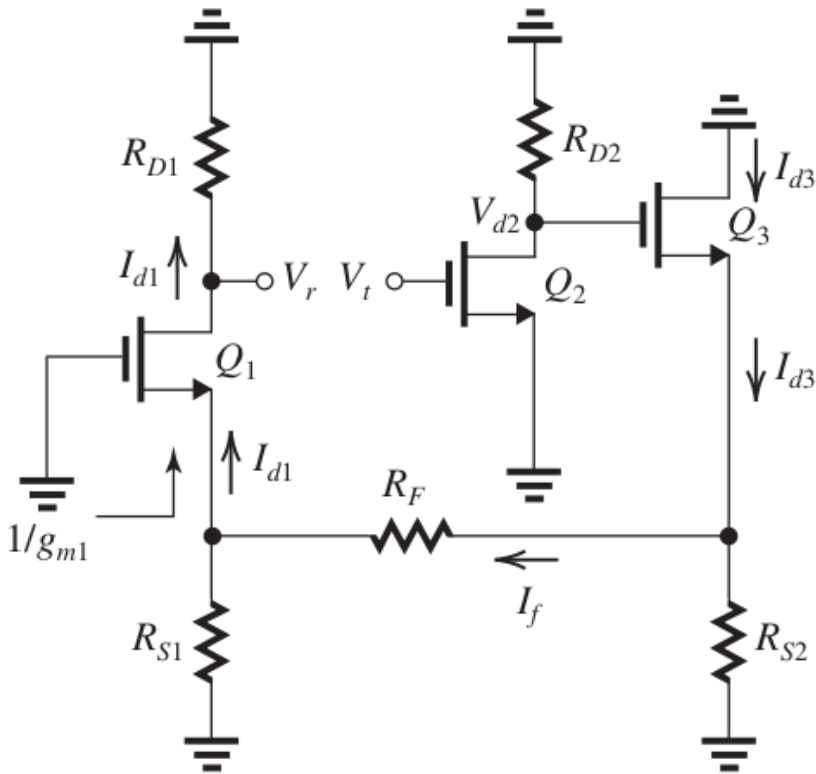

**Figure 1**

Figure 1 shows the circuit for determining the loop gain. Observe that we have broken the loop at the gate of  $Q_2$  where the input resistance is infinite, obviating the need for adding a termination resistance. Also, observe that as usual we have set  $V_s = 0$ . To determine the loop gain

$$A\beta \equiv -\frac{V_r}{V_t}$$

we write the following equations:

$$V_{d2} = -g_{m2}R_{D2}V_t \tag{1}$$

$$I_{d3} = \frac{V_{d2}}{\frac{1}{g_{m3}} + \left\{ R_{S2} \parallel \left[ R_F + \left( R_{S1} \parallel \frac{1}{g_{m1}} \right) \right] \right\}} \tag{2}$$



$$I_f = I_{d3} \frac{R_{S2}}{\left[ R_F + \left( R_{S1} \parallel \frac{1}{g_{m1}} \right) \right] + R_{S2}} \quad (3)$$

$$I_{d1} = I_f \frac{R_{S1}}{R_{S1} + \frac{1}{g_{m1}}} \quad (4)$$

$$V_r = I_{d1} R_{D1} \quad (5)$$

Substituting the numerical values in (1)–(5), we obtain

$$V_{d2} = -4 \times 10V_t = -40V_t \quad (6)$$

$$I_{d3} = \frac{V_{d2}}{\frac{1}{4} + \left\{ 0.1 \parallel \left[ 0.9 + \left( 0.1 \parallel \frac{1}{4} \right) \right] \right\}}$$

$$I_{d3} = 2.935V_{d2} \quad (7)$$

$$I_f = I_{d3} \frac{0.1}{\left[ 0.9 + \left( 0.1 \parallel \frac{1}{4} \right) \right] + 0.1}$$

$$I_f = 0.0933I_{d3} \quad (8)$$

$$I_{d1} = I_f \frac{0.1}{0.1 + \frac{1}{4}} = 0.286I_f \quad (9)$$

$$V_r = 10I_{d1} \quad (10)$$

Combining (6)–(10) gives

$$V_r = -31.33V_t$$

$$\Rightarrow A\beta = 31.33$$

$$A = \frac{A\beta}{\beta} = \frac{31.33}{0.1} = 313.3 \text{ V/V}$$

$$A_f = \frac{A}{1 + A\beta}$$

$$= \frac{313.3}{1 + 31.33} = 9.7 \text{ V/V}$$

Thus,  $A_f$  is 0.3 V/V lower than the ideal value of 10 V/V, a difference of  $-3\%$ . The circuit could be adjusted to make  $A_f$  exactly 10 by changing  $\beta$  through varying  $R_F$ . Specifically,

$$10 = \frac{313.3}{1 + 313.3\beta}$$

$$\Rightarrow \beta = 0.0968$$

But,

$$\beta = \frac{R_{S1}}{R_{S1} + R_F}$$

$$0.0968 = \frac{0.1}{0.1 + R_F}$$

$$\Rightarrow R_F = 933 \Omega$$

(an increase of 33  $\Omega$ ).

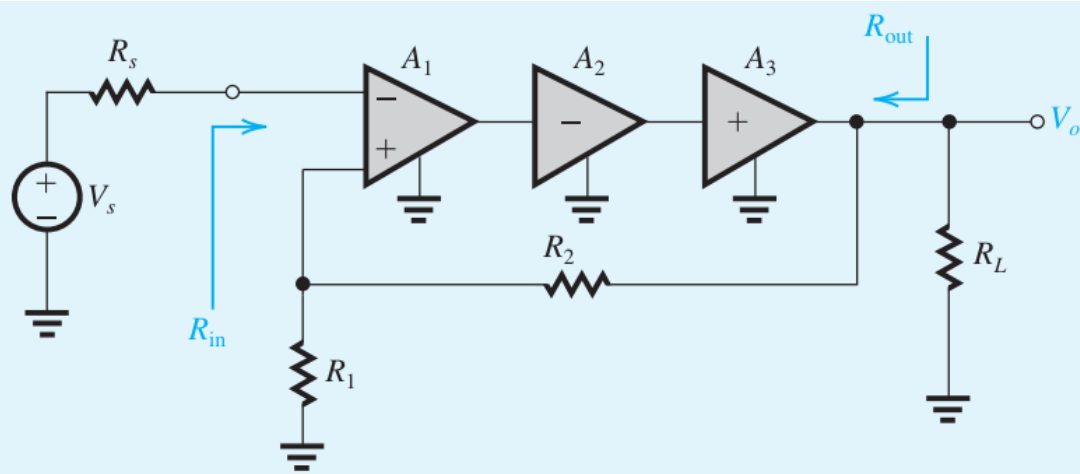


Figure P11.45

**D \*11.45** Figure P11.45 shows a three-stage feedback amplifier:

$A_1$  has an  $82\text{-k}\Omega$  differential input resistance, a  $20\text{-V/V}$  open-circuit differential voltage gain, and a  $3.2\text{-k}\Omega$  output resistance.

$A_2$  has a  $5\text{-k}\Omega$  input resistance, a  $20\text{-mA/V}$  short-circuit transconductance, and a  $20\text{-k}\Omega$  output resistance.

$A_3$  has a  $20\text{-k}\Omega$  input resistance, unity open-circuit voltage gain, and a  $1\text{-k}\Omega$  output resistance.

The feedback amplifier feeds a  $1\text{-k}\Omega$  load resistance and is fed by a signal source with a  $9\text{-k}\Omega$  resistance.

- Show that the feedback is negative.
- If  $R_1 = 20\text{ k}\Omega$ , find the value of  $R_2$  that results in a closed-loop gain  $V_o/V_s$  that is ideally  $5\text{ V/V}$ .
- Supply the small-signal equivalent circuit.
- Sketch the  $A$  circuit and determine  $A$ .
- Find  $\beta$  and the amount of feedback.
- Find the closed-loop gain  $A_f \equiv V_o/V_s$ .
- Find the feedback amplifier's input resistance  $R_{in}$ .
- Find the feedback amplifier's output resistance  $R_{out}$ .
- If the high-frequency response of the open-loop gain  $A$  is dominated by a pole at  $100\text{ Hz}$ , what is the upper  $3\text{-dB}$  frequency of the closed-loop gain?
- If for some reason  $A_1$  drops to half its nominal value, what is the percentage change in  $A_f$ ?

**10.40** (a) Refer to Fig. P10.40. If  $V_s$  increases, the output of  $A_1$  will decrease and this will cause the output of  $A_2$  to increase. This, in turn, causes the output of  $A_3$ , which is  $V_o$ , to increase. A portion of the positive increment in  $V_o$  is fed back to the positive input terminal of  $A_1$  through the voltage divider  $(R_2, R_1)$ . The increased voltage at the positive input terminal of  $A_1$  counteracts the originally assumed increase at the negative input terminal, verifying that the feedback is negative.

$$(b) A_f|_{\text{ideal}} = \frac{1}{\beta}$$

where

$$\beta = \frac{R_1}{R_1 + R_2}$$

Thus, to obtain an ideal closed-loop gain of  $5\text{ V/V}$  we need  $\beta = 0.2$ :

$$0.2 = \frac{20}{20 + R_2}$$

$$\Rightarrow R_2 = 80\text{ k}\Omega$$

(c) Figure 1 on the next page shows the small-signal equivalent circuit of the feedback amplifier.

(d) Figure 2 on the next page shows the  $A$  circuit and the  $\beta$  circuit together with the determination of its loading effects,  $R_{11}$ , and  $R_{22}$ . We can write

$$\frac{V_1}{V_i} = -\frac{82}{82 + 9 + 16} = -0.766\text{ V/V}$$

$$V_2 = 20V_1 \times \frac{5}{3.2 + 5} = 12.195V_1$$

$$V_3 = -20V_2(20 \parallel 20) = -200V_2$$

This figure belongs to Problem 10.40, part (c).

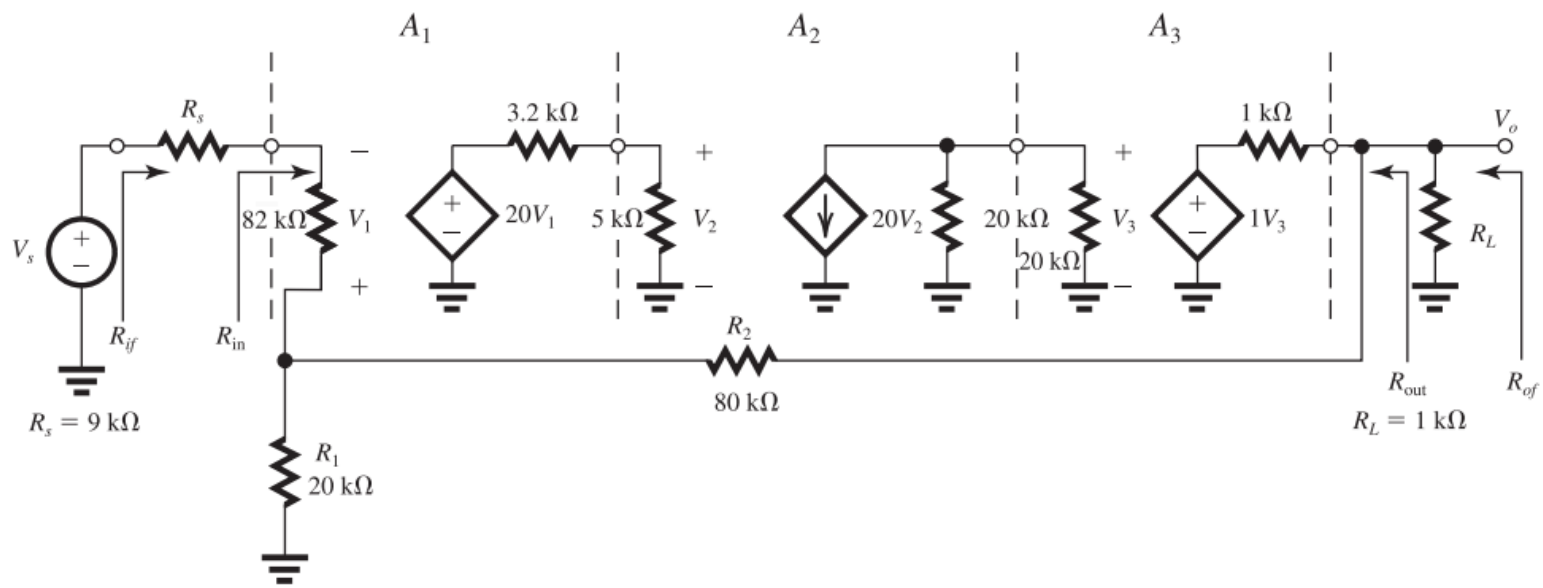


Figure 1

This figure belongs to Problem 10.40, part (d).

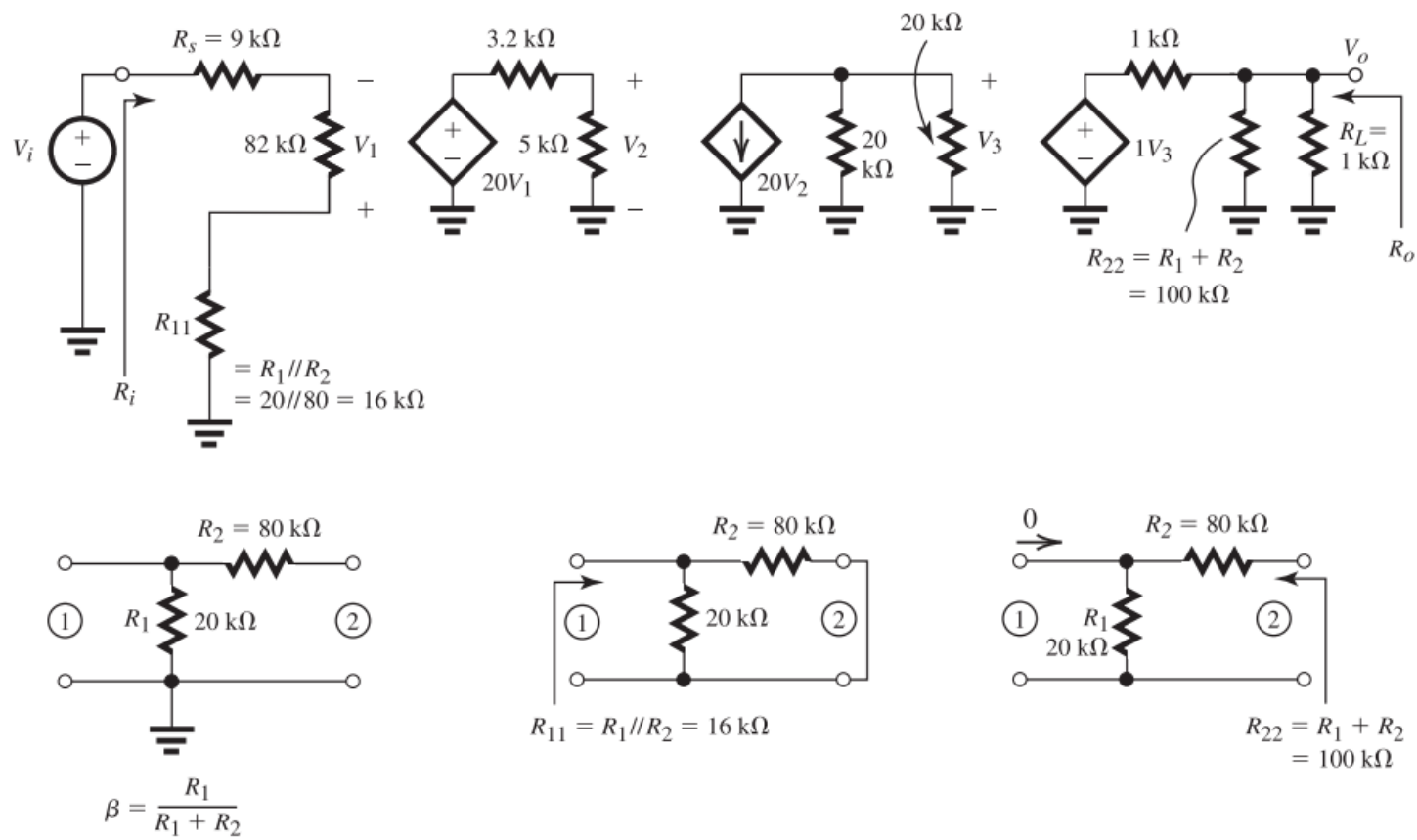


Figure 2

$$V_o = V_3 \frac{1 \parallel 100}{(1 \parallel 100) + 1} = 0.497V_3$$

Thus,

$$A \equiv \frac{V_o}{V_i} = 0.497 \times -200 \times 12.195 \times -0.766$$

$$= 928.5 \text{ V/V}$$

$$(e) \beta = \frac{20}{20 + 80} = 0.2 \text{ V/V}$$

$$1 + A\beta = 1 + 928.5 \times 0.2 = 186.7$$

$$(f) A_f \equiv \frac{V_o}{V_s} = \frac{A}{1 + A\beta}$$

$$= \frac{928.5}{186.7} = 4.97 \text{ V/V}$$

which is nearly equal to the ideal value of 5 V/V.

(g) From the A circuit,

$$R_i = 9 + 82 + 16 = 107 \text{ k}\Omega$$

$$R_{if} = R_i(1 + A\beta)$$

$$= 107 \times 186.7 = 19.98 \text{ M}\Omega$$

$$R_{in} = R_{if} - R_s \simeq 19.98 \text{ M}\Omega$$

(h) From the A circuit,

$$R_o = R_L \parallel R_{22} \parallel 1 \text{ k}\Omega$$

$$= 1 \parallel 100 \parallel 1 = 497.5 \Omega$$

$$R_{of} = \frac{R_o}{1 + A\beta} = \frac{497.5}{186.7} = 2.66 \Omega$$

$$R_{\text{out}} \parallel R_L = R_{of}$$

$$R_{\text{out}} \parallel 1000 = 2.66 \, \Omega$$

$$R_{\text{out}} \simeq 2.66 \, \Omega$$

$$(i) \, f_{Hf} = f_H (1 + A\beta)$$

$$= 100 \times 186.7$$

$$= 18.67 \, \text{kHz}$$

(j) If  $A_1$  drops to half its nominal value,  $A$  will drop to half its nominal value:

$$A = \frac{1}{2} \times 928.5 = 464.25$$

and  $A_f$  becomes

$$A_f = \frac{464.25}{1 + 464.25 \times 0.2} = 4.947 \, \text{V/V}$$

Thus, the percentage change in  $A_f$  is

$$= \frac{4.947 - 4.97}{4.97} = -0.47\%$$

**D 11.53** The transconductance amplifier in Fig. P11.53 utilizes a differential amplifier with gain  $\mu$  and a very high input resistance. The differential amplifier drives a transistor  $Q$  characterized by its  $g_m$  and  $r_o$ . A resistor  $R_F$  senses the output current  $I_o$ .

- For  $A\beta \gg 1$ , find an approximate expression for the closed-loop transconductance  $A_f \equiv I_o/V_s$ . Hence, select a value for  $R_F$  that results in  $A_f \simeq 5$  mA/V.
- Find the  $A$  circuit and derive an expression for  $A$ . Evaluate  $A$  for the case  $\mu = 1000$  V/V,  $g_m = 2$  mA/V,  $r_o = 20$  k $\Omega$ , and the value of  $R_F$  you selected in (a).
- Give an expression for  $A\beta$  and evaluate its value and that of  $1 + A\beta$ .
- Find the closed-loop gain  $A_f$  and compare to the value you designed for in (a) above.
- Find expressions and values for  $R_o$  and  $R_{of}$ . [Hint: The resistance looking into the drain of a MOSFET with a resistance  $R_s$  in its source is  $(r_o + R_s + g_m r_o R_s)$ .]

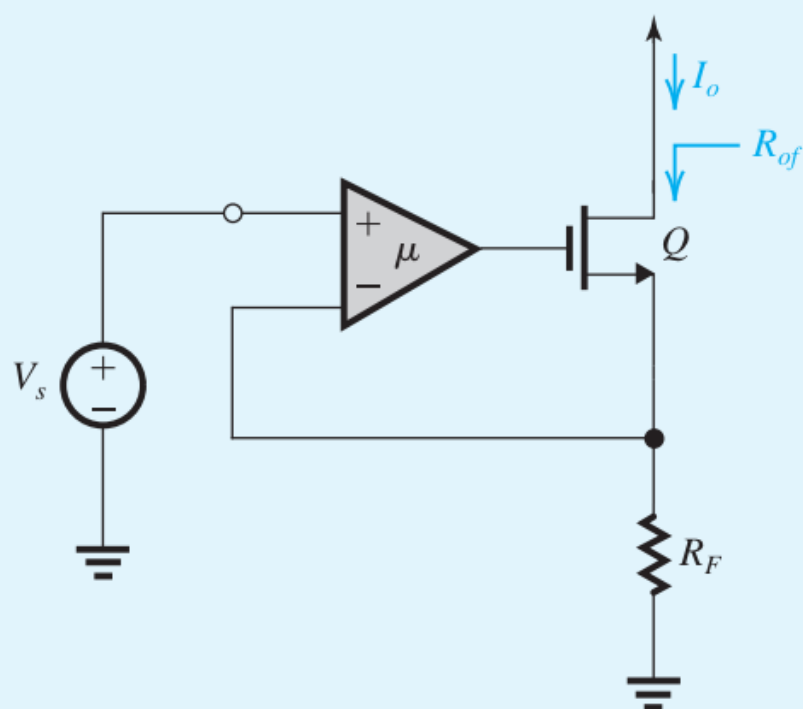


Figure P11.53

**10.49** (a) The  $\beta$  circuit is shown in Fig. 1:

$$\beta = R_F$$

For  $A\beta \gg 1$ ,  $A_f \equiv I_o/V_s$  approaches the ideal value

$$A_f|_{\text{ideal}} = \frac{1}{\beta} = \frac{1}{R_F}$$

To obtain  $A_f \simeq 5$  mA/V, we use

$$R_F = \frac{1}{5} = 0.2 \text{ k}\Omega = 200 \Omega$$

(b) Determining the loading effects of the  $\beta$  network is illustrated in Fig. 1:

$$R_{11} = R_{22} = R_F$$

Figure 2 (next page) shows the  $A$  circuit. An expression for  $A \equiv I_o/V_i$  can be derived as follows:

$$V_1 = V_i \quad (1)$$

$$V_{gs} = \mu V_1 - I_o R_F \quad (2)$$

$$I_o = g_m V_{gs} \frac{r_o}{r_o + R_F} \quad (3)$$

Combining Eqs. (1)–(3) yields

$$A \equiv \frac{I_o}{V_i} = \frac{\mu g_m r_o}{r_o + R_F + g_m r_o R_F}$$

For  $\mu = 1000$  V/V,  $g_m = 2$  mA/V,  $r_o = 20$  k $\Omega$ , and  $R_F = 0.2$  k $\Omega$ , we have

$$A = \frac{1000 \times 2 \times 20}{20 + 0.2 + 2 \times 20 \times 0.2} = 1418.4 \text{ mA/V}$$

$$(c) A\beta = \frac{\mu g_m r_o R_F}{r_o + R_F + g_m r_o R_F}$$

$$A\beta = 283.7$$

$$1 + A\beta = 284.7$$

$$(d) A_f \equiv \frac{I_o}{V_s} = \frac{A}{1 + A\beta}$$

$$= \frac{1418.4}{284.7} = 4.982 \text{ mA/V}$$

which is very close to the ideal value of 5 mA/V.

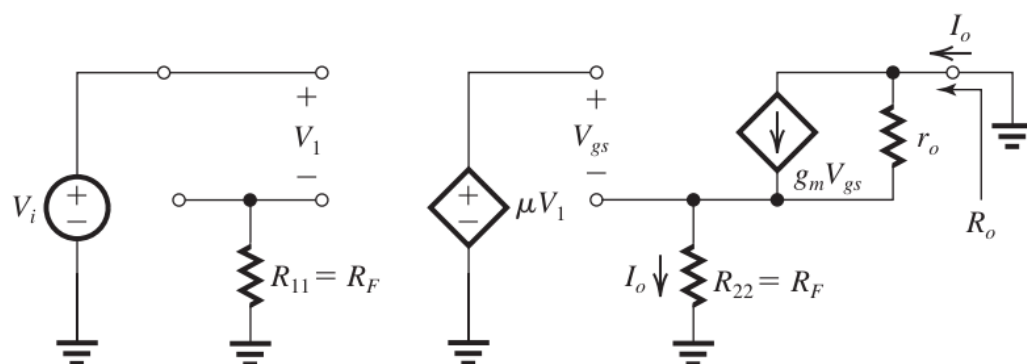


Figure 2

This figure belongs to Problem 10.49, part (b).



(e) From the A circuit in Fig. 2, we have

$$R_o = r_o + R_F + g_m r_o R_F$$

$$1 + A\beta = 1 + \frac{\mu g_m r_o R_F}{r_o + R_F + g_m r_o R_F}$$

$$R_{of} = (1 + A\beta)R_o$$

$$= r_o + R_F + g_m r_o R_F + \mu g_m r_o R_F$$

$$= r_o + R_F + (\mu + 1)g_m r_o R_F$$

$$\simeq \mu g_m r_o R_F$$

$$R_o = 20 + 0.2 + 2 \times 20 \times 0.2$$

$$= 28.2 \text{ k}\Omega$$


$$R_{of} = 20 + 0.2 + 1001 \times 2 \times 20 \times 0.2$$

$$= 20 + 0.2 + 8008 = 8028.2 \text{ k}\Omega$$

$$\simeq 8 \text{ M}\Omega$$

**\*11.54** It is required to show that the output resistance of the BJT circuit in Fig. P11.54 is given by


$$R_o = r_o + [R_e \parallel (r_\pi + R_b)] \left( 1 + g_m r_o \frac{r_\pi}{r_\pi + R_b} \right)$$

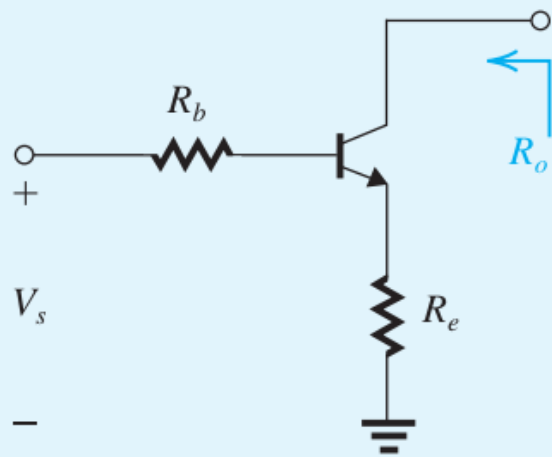

**Figure P11.54**

To derive this expression, set  $V_s = 0$ , replace the BJT with its small-signal, hybrid- $\pi$  model, apply a test voltage  $V_x$  to the collector, and find the current  $I_x$  drawn from  $V_x$  and hence  $R_o$  as  $V_x/I_x$ . Note that the bias arrangement is not shown. For the case of  $R_b = 0$ , find the maximum possible value for  $R_o$ . Note that this theoretical maximum is obtained when  $R_e$  is so large that the signal current in the emitter is nearly zero. In this case, with  $V_x$  applied and  $V_s = 0$ , what is the current in the base, in the  $g_m V_\pi$  generator, and in  $r_o$ , all in terms of  $I_x$ ? Show these currents on a sketch of the equivalent circuit with  $R_e$  set to  $\infty$ .

This figure belongs to Problem 10.50.

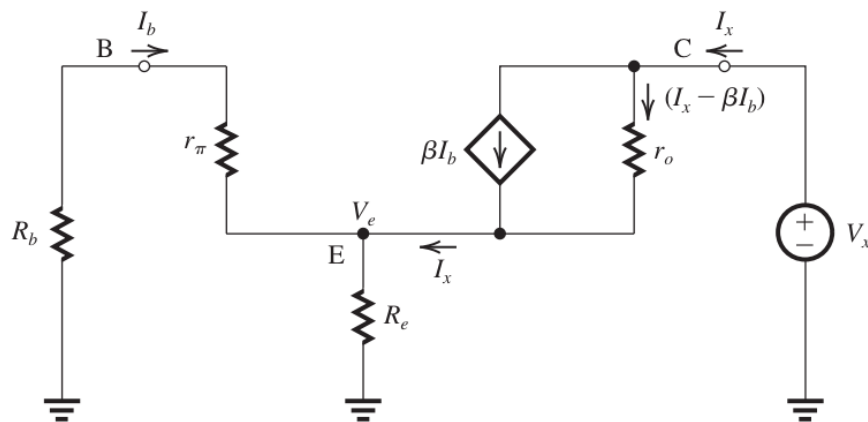

**Figure 1**

**10.50** Figure 1 on the next page shows the equivalent circuit with  $V_s = 0$  and a voltage  $V_x$  applied to the collector for the purpose of determining the output resistance  $R_o$ ,

$$R_o \equiv \frac{V_x}{I_x}$$

Some of the analysis is displayed on the circuit diagram. Since the current entering the emitter node is equal to  $I_x$ , we can write for the emitter voltage

$$V_e = I_x [R_e \parallel (r_\pi + R_b)] \quad (1)$$

The base current can be obtained using the current-divider rule applied to  $R_e$  and  $(r_\pi + R_b)$  as

$$I_b = -I_x \frac{R_e}{R_e + r_\pi + R_b} \quad (2)$$

The voltage from collector to ground is equal to  $V_x$  and can be expressed as the sum of the voltage drop across  $r_o$  and  $V_e$ ,

$$V_x = (I_x - \beta I_b) r_o + V_e$$

Substituting for  $V_e$  from (1) and for  $I_b$  from (2), we obtain

$$\begin{aligned} R_o &= \frac{V_x}{I_x} = r_o + [R_e \parallel (r_\pi + R_b)] \\ &\quad + \frac{R_e \beta r_o}{R_e + r_\pi + R_b} \\ &= r_o + [R_e \parallel (r_\pi + R_b)] \left[ 1 + r_o \frac{\beta}{r_\pi + R_b} \right] \end{aligned}$$

Since  $\beta = g_m r_\pi$ , we obtain

$$R_o = r_o + [R_e \parallel (r_\pi + R_b)] \left[ 1 + g_m r_o \frac{r_\pi}{r_\pi + R_b} \right] \quad \text{Q.E.D.}$$

For  $R_b = 0$ ,

$$R_o = r_o + (R_e \parallel r_\pi)(1 + g_m r_o)$$

The maximum value of  $R_o$  will be obtained when  $R_e \gg r_\pi$ . If  $R_e$  approaches infinity (zero signal current in the emitter),  $R_o$  approaches the theoretical maximum:

$$\begin{aligned} R_{o\max} &= r_o + r_\pi(1 + g_m r_o) \\ &= r_o + r_\pi + \beta r_o \\ &\simeq \beta r_o \end{aligned} \tag{3}$$

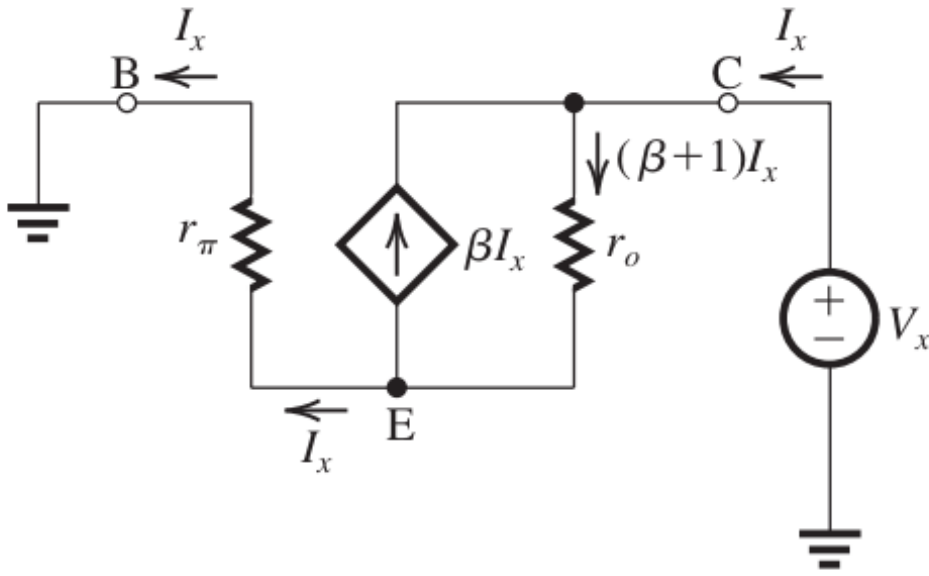


Figure 2

The situation that pertains in the circuit when  $R_e = \infty$  is illustrated in Fig. 2. Observe that since the signal current in the emitter is zero, the base current will be equal to the collector current ( $I_x$ ) and in the direction indicated. The controlled-source current will be  $\beta I_x$ , and this current adds to  $I_x$  to provide a current  $(\beta + 1)I_x$  in the output resistance  $r_o$ . A loop equation takes the form

$$V_x = (\beta + 1)I_x r_o + I_x r_\pi$$

and thus

$$R_o \equiv \frac{V_x}{I_x} = r_\pi + (\beta + 1)r_o$$

which is identical to the result in Eq. (3).

**11.65** The feedback transresistance amplifier in Fig. P11.65 utilizes two identical MOSFETs biased by ideal current sources  $I = 0.4 \text{ mA}$ . The MOSFETs are sized to operate at  $V_{OV} = 0.2 \text{ V}$  and have  $V_t = 0.5 \text{ V}$  and  $V_A = 16 \text{ V}$ . The feedback resistance  $R_F = 10 \text{ k}\Omega$ .

- If  $I_s$  has a zero dc component, find the dc voltage at the input, at the drain of  $Q_1$ , and at the output.
- Find  $g_m$  and  $r_o$  of  $Q_1$  and  $Q_2$ .
- Provide the  $A$  circuit and derive an expression for  $A$  in terms of  $g_{m1}$ ,  $r_{o1}$ ,  $g_{m2}$ ,  $r_{o2}$ , and  $R_F$ .
- What is  $\beta$ ? Give an expression for the loop gain  $A\beta$  and the amount of feedback  $(1 + A\beta)$ .
- Derive an expression for  $A_f$ .
- Derive expressions for  $R_i$ ,  $R_{in}$ ,  $R_o$ , and  $R_{out}$ .
- Evaluate  $A$ ,  $\beta$ ,  $A\beta$ ,  $A_f$ ,  $R_i$ ,  $R_o$ ,  $R_{in}$ , and  $R_{out}$  for the component values given.

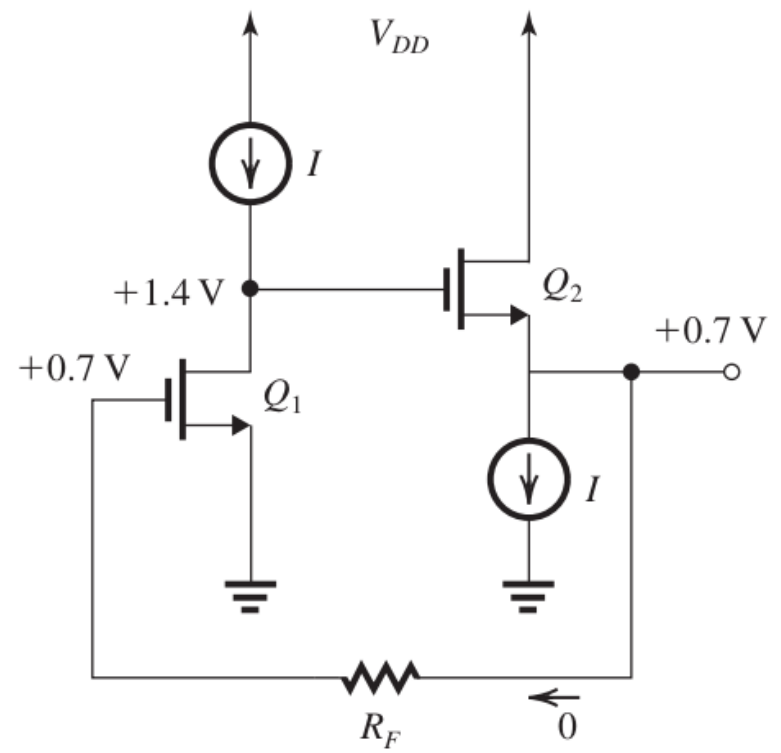


Figure 1

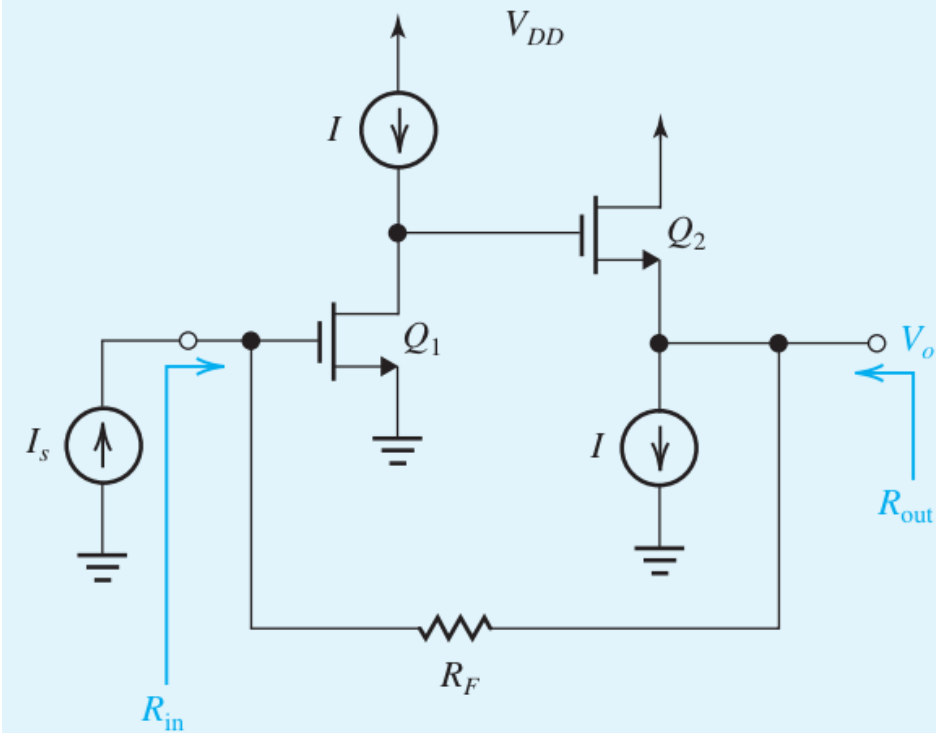


Figure P11.65

- See Figure 1.

$$V_{G1} = V_{GS1} = V_t + V_{OV} \\ = 0.5 + 0.2 = +0.7 \text{ V}$$

(because the dc voltage across  $R_F$  is zero)

$$V_O = V_{G1}$$

$$V_O = +0.7 \text{ V}$$

$$V_{D1} = V_O + V_{GS2} \\ = 0.7 + 0.5 + 0.2 \\ = +1.4 \text{ V}$$

$$(b) \quad g_{m1,2} = \frac{2I}{V_{OV}} = \frac{2 \times 0.4}{0.2} = 4 \text{ mA/V}$$

$$r_{o1,2} = \frac{V_A}{I} = \frac{16 \text{ V}}{0.4 \text{ mA}} = 40 \text{ k}\Omega$$

- Figure 2 on the next page shows the  $\beta$  circuit and the determination of its loading effects,

$$R_{11} = R_{22} = R_F$$

Figure 2 shows also the  $A$  circuit. We can write

$$V_{g1} = I_i R_i \quad (1)$$

where

$$R_i = R_{11} = R_F \quad (2)$$

$$V_{d1} = -g_{m1} r_{o1} V_{g1} \quad (3)$$

This figure belongs to Problem 10.58, part (c).

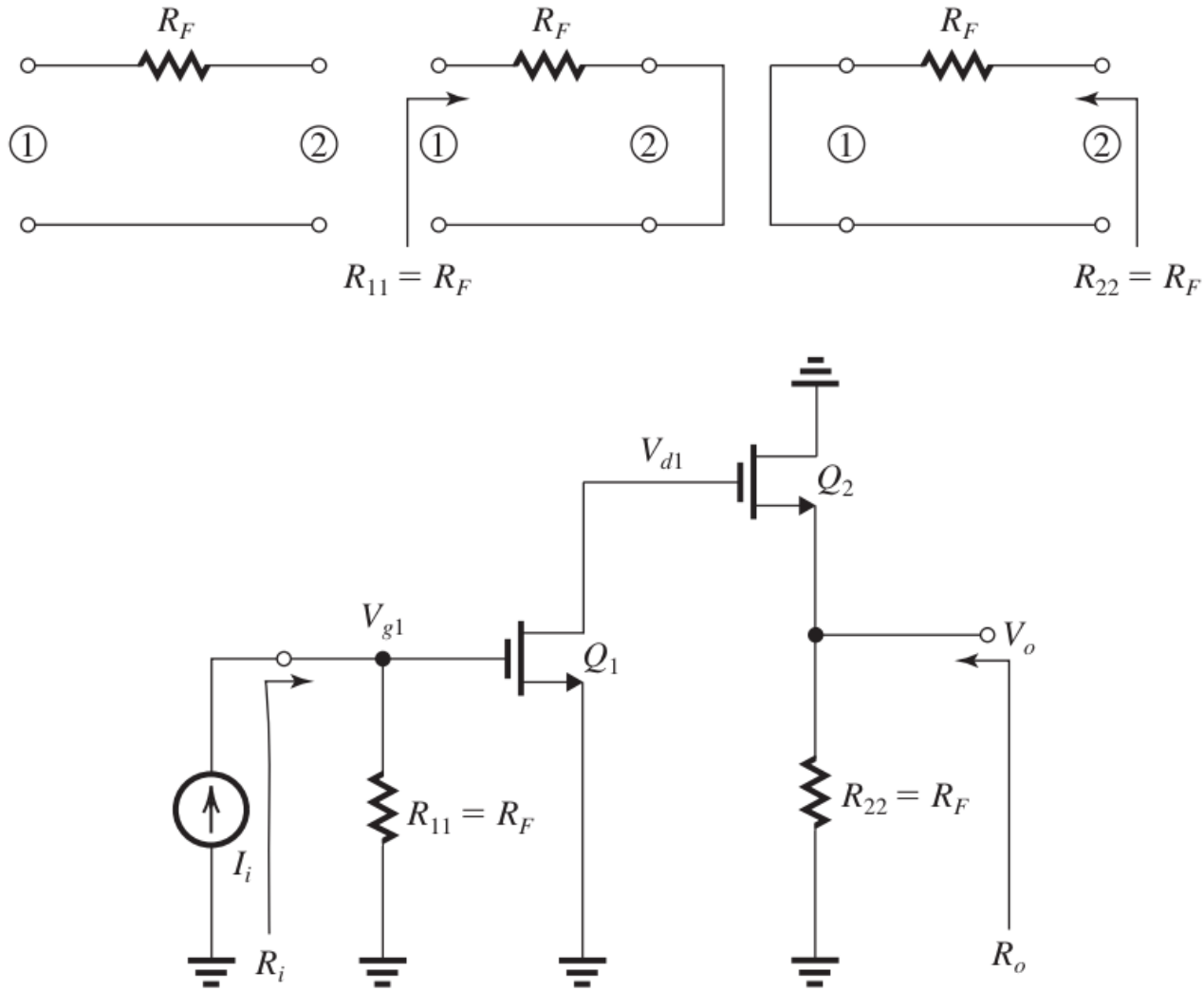


Figure 2

$$\frac{V_o}{V_{d1}} = \frac{R_{22} \parallel r_{o2}}{(R_{22} \parallel r_{o2}) + \frac{1}{g_{m2}}} \quad (4)$$

Combining Eqs. (1)–(4) results in

$$A \equiv \frac{V_o}{I_i} = -g_{m1} r_{o1} R_F \frac{R_F \parallel r_{o2}}{(R_F \parallel r_{o2}) + 1/g_{m2}}$$

(d)

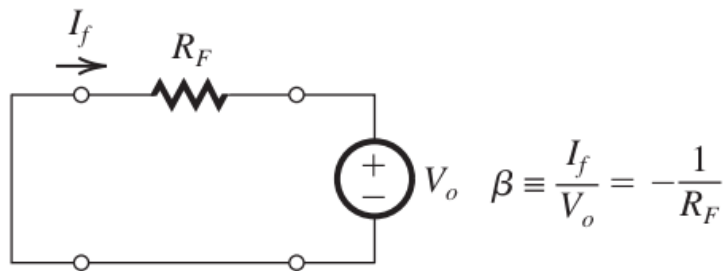


Figure 3

From Fig. 3 we see that

$$\beta = -\frac{1}{R_F}$$

$$A\beta = g_{m1} r_{o1} \frac{R_F \parallel r_{o2}}{(R_F \parallel r_{o2}) + 1/g_{m2}}$$

$$1 + A\beta = 1 + g_{m1} r_{o1} \frac{R_F \parallel r_{o2}}{(R_F \parallel r_{o2}) + 1/g_{m2}}$$

$$(e) A_f \equiv \frac{V_o}{I_s} = \frac{A}{1 + A\beta}$$

$$= -\frac{g_{m1} r_{o1} R_F (R_F \parallel r_{o2})}{(R_F \parallel r_{o2}) + 1/g_{m2} + (g_{m1} r_{o1})(R_F \parallel r_{o2})}$$

$$(f) R_i = R_F$$

$$R_{in} = R_{if} = R_i / (1 + A\beta)$$

$$= R_F / \left[ 1 + g_{m1} r_{o1} \frac{R_F \parallel r_{o2}}{(R_F \parallel r_{o2}) + 1/g_{m2}} \right]$$

$$R_{out} = R_{of} = R_o / (1 + A\beta)$$

where from the A circuit we have

$$R_o = R_F \parallel r_{o2} \parallel \frac{1}{g_{m2}}$$

$$R_{out} = \left( R_F \parallel r_{o2} \parallel \frac{1}{g_{m2}} \right) /$$

$$\left[ 1 + g_{m1} r_{o1} \frac{R_F \parallel r_{o2}}{(R_F \parallel r_{o2}) + 1/g_{m2}} \right]$$

$$(g) A = -4 \times 40 \times 10 \frac{10 \parallel 40}{(10 \parallel 40) + 0.25}$$

$$= -1551.5 \text{ k}\Omega$$

$$\beta = -\frac{1}{R_F} = -\frac{1}{10 \text{ k}\Omega} = -0.1 \text{ mA/V}$$



$$A\beta = 155.15$$

$$1 + A\beta = 156.15$$

$$A_f = -\frac{1551.5}{156.15} = -9.94 \text{ k}\Omega$$

$$R_i = R_F = 10 \text{ k}\Omega$$

$$R_{\text{in}} = R_{if} = \frac{R_F}{1 + A\beta} = \frac{10,000 \text{ }\Omega}{156.15} = 64 \text{ }\Omega$$

$$R_o = R_F \parallel r_{o2} \parallel \frac{1}{g_{m2}}$$


$$R_o = 10 \parallel 40 \parallel 0.25 = 242 \text{ }\Omega$$

$$R_{\text{out}} = R_{of} = \frac{R_o}{1 + A\beta}$$


$$= \frac{242}{156.15} = 1.55 \text{ }\Omega$$

**\*11.78** The feedback current amplifier in Fig. P11.78(a) can be thought of as a “super” CG transistor. Note that rather than connecting the gate of  $Q_2$  to signal ground, an amplifier is placed between source and gate.

- If  $\mu$  is very large, what is the signal voltage at the input terminal? What is the input resistance? What is the current gain  $I_o/I_s$ ?
- For finite  $\mu$  but assuming that the input resistance of the amplifier  $\mu$  is very large, find the  $A$  circuit and derive expressions for  $A$ ,  $R_i$ , and  $R_o$ .
- What is the value of  $\beta$ ?
- Find  $A\beta$  and  $A_f$ . If  $\mu$  is large, what is the value of  $A_f$ ?
- Find  $R_{in}$  and  $R_{out}$  assuming the loop gain is large.
- The “super” CG transistor can be utilized in the cascode configuration shown in Fig. P11.78(b), where  $V_G$  is a dc bias voltage. Replacing  $Q_1$  by its small-signal model, use the analogy of the resulting circuit to that in Fig. P11.78(a) to find  $I_o$  and  $R_{out}$ .

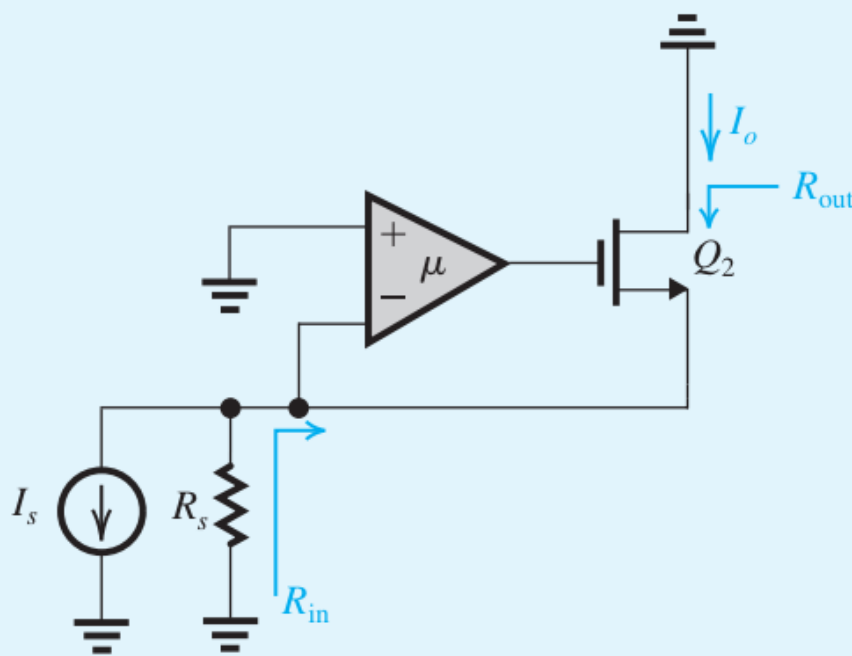

(a)

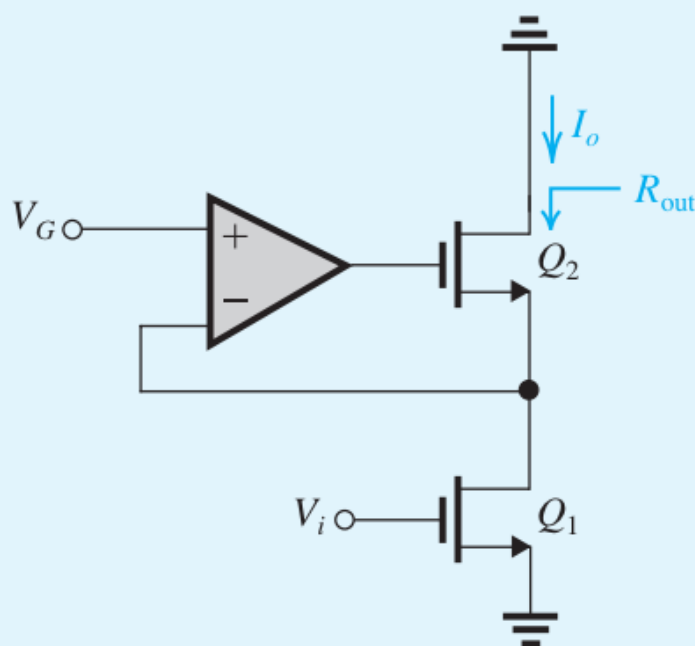

(b)

**Figure P11.78**

**10.70** (a) If  $\mu$  is a very large, a virtual ground will appear at the input terminal. Thus the input resistance  $R_{in} = V_-/I_i = 0$ . Since no current flows in  $R_s$ , or into the amplifier input terminal, all the current  $I_s$  will flow in the transistor source terminal and hence into the drain, thus

$$I_o = I_s$$

and

$$\frac{I_o}{I_s} = 1$$

(b) This is a shunt-series feedback amplifier in which the feedback circuit consists of a wire, as shown on the next page in Fig. 1. As indicated,

$$R_{11} = \infty$$

$$R_{22} = 0$$

The  $A$  circuit is shown in Fig. 2 (next page) for which we can write

$$V_{id} = -I_i(R_s \parallel R_{id})$$

$$\simeq -I_i R_s \quad (1)$$

(since  $R_{id}$  is very large)

$$V_{gs} = \mu V_{id} \quad (2)$$

$$I_o = g_{m2} V_{gs} \quad (3)$$

Combining (1)–(3), we obtain

$$A \equiv \frac{I_o}{I_i} = -\mu g_{m2} R_s$$

These figures belong to Problem 10.70, part (b).

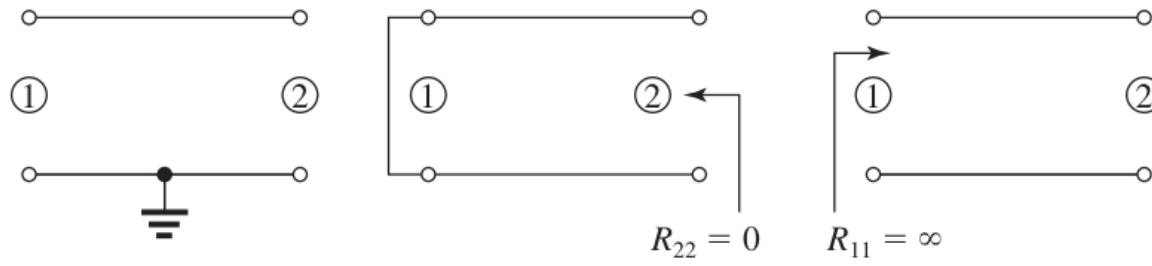


Figure 1

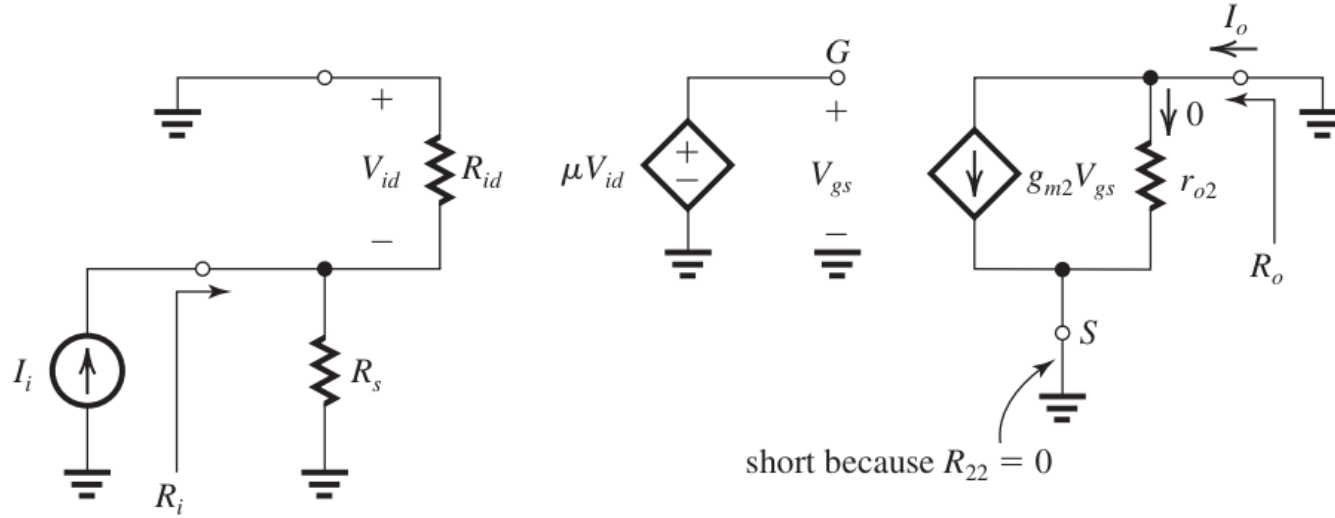


Figure 2

$$R_i = R_s$$

$$R_o = r_{o2}$$

(c)

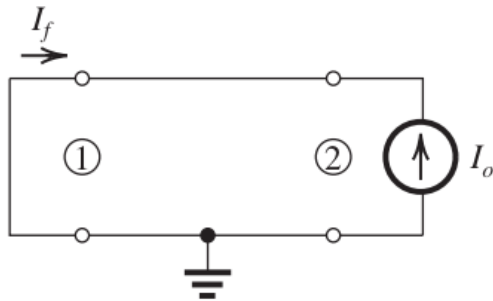


Figure 3

From Fig. 3 we find

$$\beta \equiv \frac{I_f}{I_o} = -1$$

$$(d) A\beta = \mu g_{m2} R_s$$

$$A_f = \frac{A}{1 + A\beta} = -\frac{\mu g_{m2} R_s}{1 + \mu g_{m2} R_s}$$

Note that the negative sign is due to our assumption that  $I_s$  flows into the input node (see Fig. 2 for the way  $I_i$  is applied). If instead  $I_s$  is flowing out of the input node, as indicated in Fig. P10.70, then

$$A_f \equiv \frac{I_o}{I_s} = \frac{\mu g_{m2} R_s}{1 + \mu g_{m2} R_s}$$

If  $\mu$  is large so that  $\mu g_{m2} R_s \gg 1$ ,

$$A_f \simeq 1$$

$$(e) R_{if} = \frac{R_i}{1 + A\beta}$$

$$= \frac{R_s}{\mu g_{m2} R_s}$$

$$R_{if} = R_{in} \parallel R_s$$

$$\frac{1}{R_{if}} = \frac{1}{R_{in}} + \frac{1}{R_s}$$

$$\frac{1}{R_s} + \mu g_{m2} = \frac{1}{R_{in}} + \frac{1}{R_s}$$

$$\Rightarrow R_{in} = \frac{1}{\mu g_{m2}}$$

$$R_{out} = R_{of} = R_o(1 + A\beta)$$

$$= r_{o2}(1 + \mu g_{m2} R_s)$$

(f)

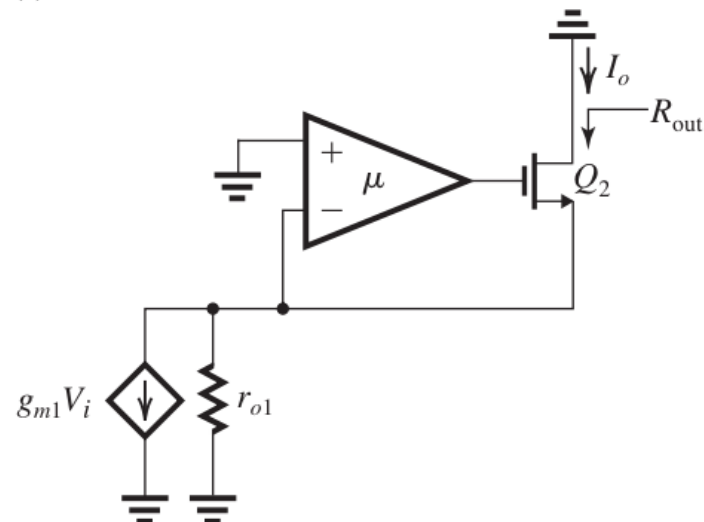


Figure 4

The circuit of the cascode amplifier in Fig. P10.70 with  $V_G$  replaced by signal ground, and  $Q_1$  replaced by its equivalent circuit at the drain (Fig. 4, previous page) looks identical to that of Fig. 10.70(a). Thus we can write

$$I_o \simeq g_{m1} v_i$$

$$R_{\text{out}} = r_{o2}(1 + \mu g_{m2} r_{o1}) = r_{o2} + \mu(g_{m2} r_{o2}) r_{o1}$$

$$\simeq \mu(g_{m2} r_{o2}) r_{o1}$$

Compared to the case of a regular cascode, we see that while  $I_o \simeq g_{m1} V_i$  as in the regular cascode, utilizing the "super" CG transistor results in increasing the output resistance by the additional factor  $\mu$ !

**11.86** Consider a feedback amplifier for which the open-loop gain  $A(s)$  is given by

$$A(s) = \frac{10,000}{(1 + s/10^4)(1 + s/10^5)^2}$$

If the feedback factor  $\beta$  is independent of frequency, find the frequency at which the phase shift is  $180^\circ$ , and find the critical value of  $\beta$  at which oscillation will commence.

$$\mathbf{10.77} \quad A(s) = \frac{10^4}{\left(1 + \frac{s}{10^4}\right) \left(1 + \frac{s}{10^5}\right)^2}$$

$$A(j\omega) = \frac{10^4}{\left(1 + j\frac{\omega}{10^4}\right) \left(1 + j\frac{\omega}{10^5}\right)^2}$$

$$\phi = -\tan^{-1}\left(\frac{\omega}{10^4}\right) - 2 \tan^{-1}\left(\frac{\omega}{10^5}\right)$$

$$-180 = -\tan^{-1}\left(\frac{\omega_{180}}{10^4}\right) - 2 \tan^{-1}\left(\frac{\omega_{180}}{10^5}\right)$$

By trial and error we find

$$\omega_{180} = 1.095 \times 10^5 \text{ rad/s}$$

At this frequency,

$$\begin{aligned} |A| &= \frac{10^4}{\sqrt{1 + 10.95^2} \sqrt{1 + 1.095^2}} \\ &= 413.6 \end{aligned}$$

For stable operation,

$$|A|\beta_{cr} < 1$$

$$\beta_{cr} < 2.42 \times 10^{-3}$$

Thus, oscillation will commence for

$$\beta \geq 2.42 \times 10^{-3}$$



**\*11.89** An amplifier having a low-frequency gain of  $10^4$  and poles at  $10^4$  Hz and  $10^5$  Hz is operated in a closed negative-feedback loop with a frequency-independent  $\beta$ .

- For what value of  $\beta$  do the closed-loop poles become coincident? At what frequency?
- What is the low-frequency, closed-loop gain corresponding to the situation in (a)? What is the value of the closed-loop gain at the frequency of the coincident poles?
- What is the value of  $Q$  corresponding to the situation in (a)?
- If  $\beta$  is increased by a factor of 10, what are the new pole locations? What is the corresponding pole  $Q$ ?

**10.82** (a) The closed-loop poles become coincident when  $Q = 0.5$ . Using Eq. (10.70), we obtain

$$Q = \frac{\sqrt{(1 + A_0\beta)\omega_{P1}\omega_{P2}}}{\omega_{P1} + \omega_{P2}}$$

$$0.5 = \frac{\sqrt{(1 + A_0\beta)\omega_{P1}\omega_{P2}}}{\omega_{P1} + \omega_{P2}}$$

$$\Rightarrow 1 + A_0\beta = 0.5^2 \frac{(\omega_{P1} + \omega_{P2})^2}{\omega_{P1}\omega_{P2}}$$

$$= 0.5^2 \times \frac{(2\pi)^2(10^4 + 10^5)^2}{(2\pi)^2 \times 10^4 \times 10^5}$$

$$= 0.5^2 \times \frac{11^2}{10} = 3.025$$

$$\beta = 2.025 \times 10^{-4}$$

$$\omega_c = \frac{1}{2}(\omega_{P1} + \omega_{P2})$$

$$= \frac{1}{2} \times 2\pi(f_{P1} + f_{P2})$$

$$f_c = \frac{1}{2} \times (10^4 + 10^5) = 5.5 \times 10^4 \text{ Hz}$$

$$(b) A_f(0) = \frac{A_0}{1 + A_0\beta}$$

$$= \frac{10^4}{1 + 2.205 \times 10^{-4} \times 10^4} = 3306 \text{ V/V}$$

$$A_f(s) = \frac{A(s)}{1 + A(s)\beta}$$

where

$$A(s) = \frac{A_0}{\left(1 + \frac{s}{\omega_{P1}}\right)\left(1 + \frac{s}{\omega_{P2}}\right)}$$

$$A_f(s) = \frac{A_0}{\left(1 + \frac{s}{\omega_{P1}}\right)\left(1 + \frac{s}{\omega_{P2}}\right) + A_0\beta}$$

$$= \frac{A_0}{(1 + A_0\beta) + s\left(\frac{1}{\omega_{P1}} + \frac{1}{\omega_{P2}}\right) + \frac{s^2}{\omega_{P1}\omega_{P2}}}$$

$$A_f(j\omega) = \frac{A_0}{(1 + A_0\beta) + j\left(\frac{\omega}{\omega_{P1}} + \frac{\omega}{\omega_{P2}}\right) - \left(\frac{\omega}{\omega_{P1}}\right)\left(\frac{\omega}{\omega_{P2}}\right)}$$

$$A_f(j\omega_c) = \frac{10^4}{3.025 + j(5.5 + 0.55) - 5.5 \times 0.55}$$

$$A_f(j\omega_c) = \frac{10^4}{j 6.05}$$

$$|A_f|(j\omega_c) = \frac{10^4}{6.05} = 1653 \text{ V/V}$$

(c)  $Q = 0.5$ .

(d) If  $\beta = 2.025 \times 10^{-3}$  V/V. Using Eq. (10.68), we obtain

$$s = -\frac{1}{2} \times 2\pi(10^4 + 10^5)$$

$$\pm \frac{1}{2} \times$$

$$2\pi\sqrt{(10^4 + 10^5)^2 - 4(1 + 10^4 \times 2.025 \times 10^{-3}) \times 10^4 \times 10^5}$$

$$\frac{s}{2\pi} = -5.5 \times 10^4$$

$$\pm 0.5\sqrt{121 \times 10^8 - 4 \times 21.25 \times 10^9}$$

$$= -5.5 \times 10^4 \pm 0.5 \times 10^4 \sqrt{121 - 40 \times 21.25}$$

$$= -5.5 \times 10^4 \pm j0.5 \times 10^4 \times 27$$

$$= (-5.5 \pm j13.25) \times 10^4 \text{ Hz}$$

Using Eq. (10.70), we obtain

$$Q = \frac{\sqrt{(1 + 10^4 \times 2.025 \times 10^{-3})10^4 \times 10^5}}{10^4 + 10^5}$$

$$= 1.325$$

**SIM \*\*11.106** The op amp in the circuit of Fig. P11.106 has an open-loop gain of  $10^5$  and a single-pole rolloff with  $\omega_{3dB} = 10 \text{ rad/s}$ .

- Sketch a Bode plot for the loop gain.
- Find the frequency at which  $|A\beta| = 1$ , and find the corresponding phase margin.
- Find the closed-loop transfer function, including its zero and poles. Sketch a pole-zero plot. Sketch the magnitude of the transfer function versus frequency, and label the important parameters on your sketch.

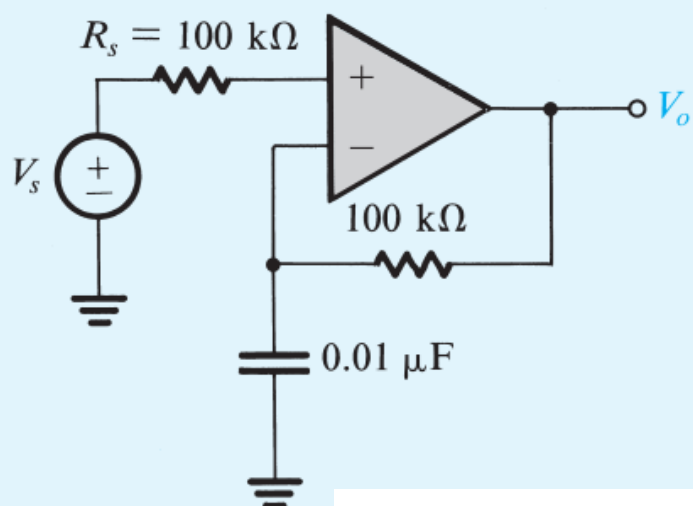


Figure P11.106

$$A(s)\beta(s) = -\frac{V_r}{V_t}$$

$$= A(s) \frac{1/sC}{R + 1/sC}$$

$$A(s)\beta(s) = \frac{10^5}{1 + \frac{s}{10}} \frac{1}{1 + sCR}$$

$$CR = 0.01 \times 10^{-6} \times 100 \times 10^3 = 10^{-3} \text{ s}$$

$$A(s)\beta(s) = \frac{10^5}{\left(1 + \frac{s}{10}\right) \left(1 + \frac{s}{10^3}\right)}$$

(a) Bode plots for the magnitude and phase of  $A\beta$  are shown in Fig. 2. From the magnitude plot we find the frequency  $f_1$  at which  $|A\beta| = 1$  is

$$f_1 = 3.16 \times 10^4 \text{ Hz}$$

(b) From the phase plot we see that the phase at  $f_1$  is  $180^\circ$  and thus the phase margin is zero. A more exact value for the phase margin can be obtained as follows:

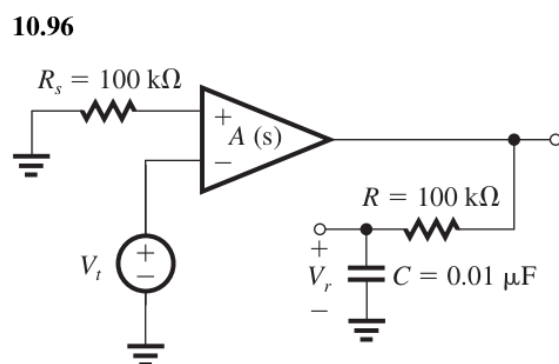


Figure 1

This figure belongs to Problem 10.96, part (a).

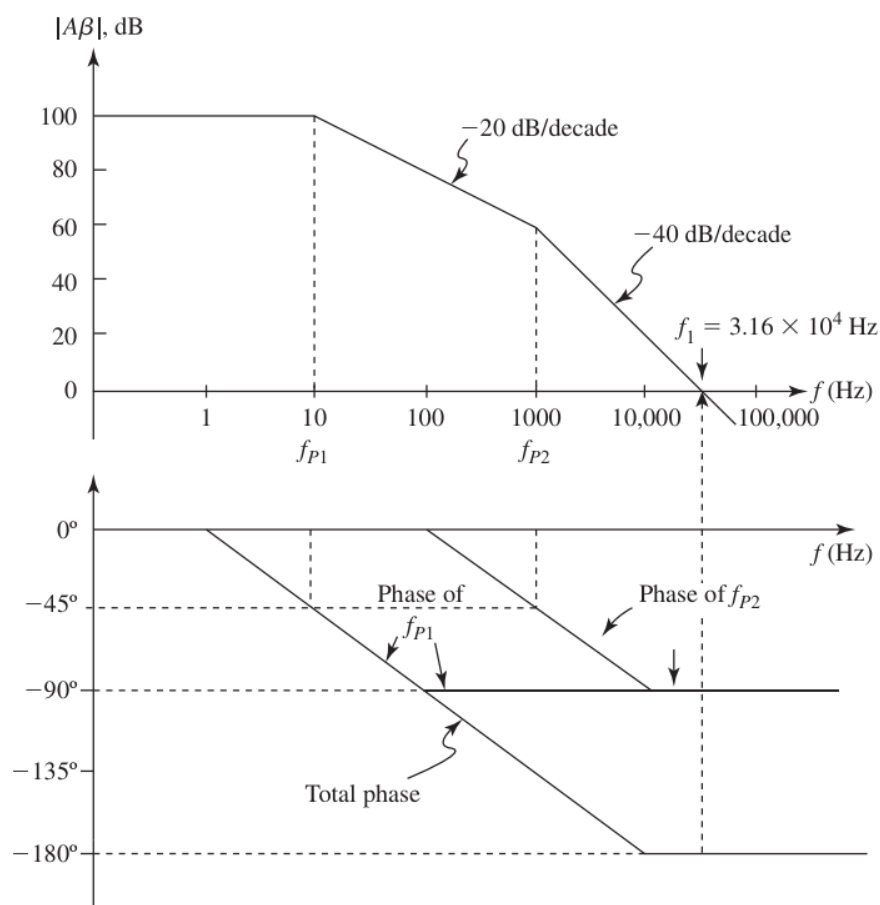


Figure 2

$$\theta(f_1) = -\tan^{-1} \frac{3.16 \times 10^4}{10} - \tan^{-1} \frac{3.16 \times 10^4}{10^3}$$

$$= -89.98 - 88.19 = -178.2$$

Thus the phase margin is  $1.8^\circ$ .

$$(c) A_f(s) = \frac{A(s)}{1 + A(s)\beta(s)}$$

$$= \frac{10^5 / \left(1 + \frac{s}{10}\right)}{1 + \frac{10^5}{\left(1 + \frac{s}{10}\right)\left(1 + \frac{s}{10^3}\right)}}$$

$$= \frac{10^5 \left(1 + \frac{s}{10^3}\right)}{10^5 + \left(1 + \frac{s}{10}\right)\left(1 + \frac{s}{10^3}\right)}$$

$$= \frac{\left(1 + \frac{s}{10^3}\right)}{1 + 10^{-5}(1 + 0.101s + 0.0001s^2)}$$

At  $s = 0$ ,

$$A_f \simeq 1$$

The transmission zero is

$$s_Z = -10^3 \text{ rad/s}$$

The poles are the roots of

$$10^{-9}s^2 + 1.01 \times 10^{-6}s + 1 = 0$$

which are

$$s = (-0.505 \pm j31.62) \times 10^3 \text{ rad/s}$$

The poles and zero are shown in Fig. 3.

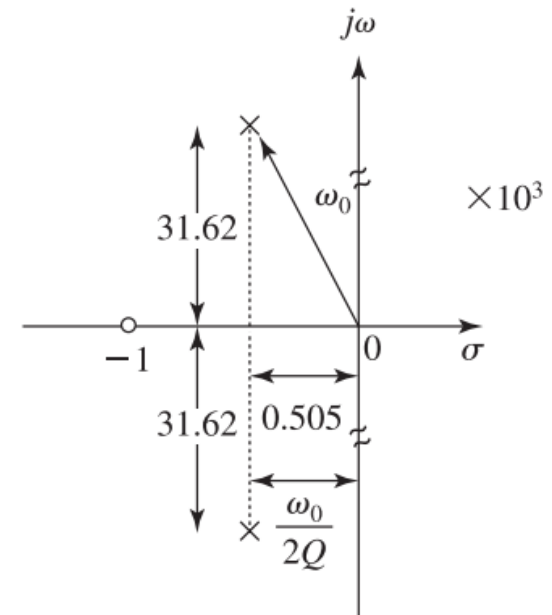


Figure 3

The pair of complex-conjugate poles have

$$\omega_0 \simeq 31.62 \text{ krad/s}$$

$$Q = 31.3$$

Thus, the response is very peaky, as shown in Fig. 4.

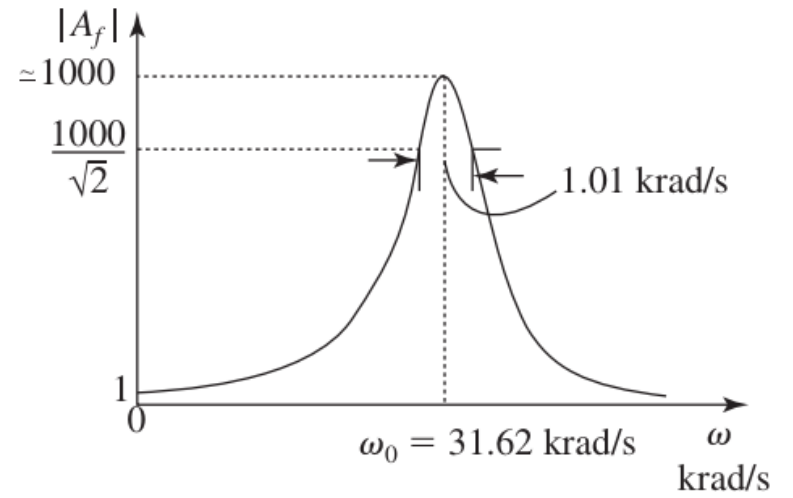


Figure 4