 



**2.22** The circuit in Fig. P2.22 is frequently used to provide an output voltage  $v_o$  proportional to an input signal current  $i_i$ .



**Figure P2.22**

Derive expressions for the transresistance  $R_m \equiv v_o/i_i$  and the input resistance  $R_i \equiv v_i/i_i$  for the following cases:

 - (a)  $A$  is infinite.
- (b)  $A$  is finite.



- (a) For  $A = \infty$ :  $v_i = 0$

$$v_o = -i_i R_f$$

$$R_m = \frac{v_o}{i_i} = -R_f$$


$$R_{in} = \frac{v_i}{i_i} = 0$$

- (b) For  $A$  finite:  $v_i = -\frac{v_o}{A}$ ,  $v_o = v_i - i_i R_f$

$$\Rightarrow v_o = \frac{-v_o}{A} - i_i R_f \Rightarrow R_m = \frac{v_o}{i_i} = -\frac{R_f}{1 + \frac{1}{A}}$$

$$R_i = \frac{v_i}{i_i} = \frac{R_f}{1 + A}$$

**\*2.25** Figure P2.25 shows an op amp that is ideal except for having a finite open-loop gain and is used to realize an inverting amplifier whose gain has a nominal magnitude  $G = R_2/R_1$ . To compensate for the gain reduction due to

 

**Figure P2.25**

the finite  $A$ , a resistor  $R_c$  is shunted across  $R_1$ . Show that perfect compensation is achieved when  $R_c$  is selected according to

$$\frac{R_c}{R_1} = \frac{A - G}{1 + G}$$

$$\frac{V_o}{V_i} = \frac{-R_2/R'_1}{1 + \frac{R_2/R'_1}{A}}$$

where

$$R'_1 = R_1 \parallel R_c$$

Thus,

$$\frac{1}{R'_1} = \frac{1}{R_1} + \frac{1}{R_c}$$

Substituting in Eq. (1),

$$\frac{V_o}{V_i} = -\frac{R_2}{R_1} \frac{1 + \frac{R_1}{R_c}}{1 + \frac{R_2}{R_1} + \frac{R_2}{R_c}} \frac{1}{1 + \frac{1}{A}}$$

To make  $\frac{V_o}{V_i} = -\frac{R_2}{R_1}$ , we have to make

$$\frac{R_1}{R_c} = \frac{1 + \frac{R_2}{R_1} + \frac{R_2}{R_c}}{A}$$

That is,


$$A \frac{R_1}{R_c} = 1 + G + G \frac{R_1}{R_c}$$

which yields


$$\frac{R_c}{R_1} = \frac{A - G}{1 + G} \quad \text{Q.E.D.}$$

**D 2.34** Assuming the op amp to be ideal, it is required to design the circuit shown in Fig. P2.34 to implement a current amplifier with gain  $i_L/i_I = 11$  A/A.

- Find the required value for  $R$ .
- What are the input and the output resistance of this current amplifier?
- If  $R_L = 1$  k $\Omega$  and the op amp operates in an ideal manner as long as  $v_O$  is in the range  $\pm 12$  V, what range of  $i_I$  is possible?
- If the amplifier is fed with a current source having a current of 0.2 mA and a source resistance of 10 k $\Omega$ , find  $i_L$ .

 

**Figure P2.34**

 

(a)  $v_x = -i_I \times 10$

$$i = -v_x/R = i_I(10/R)$$

$$i_L = i_I + i = i_I \left( 1 + \frac{10}{R} \right)$$

Thus,

$$\frac{i_L}{i_I} = 1 + \frac{10}{R}$$

For  $\frac{i_L}{i_I} = 11 \Rightarrow R = 1$  k $\Omega$ .

(b)  $R_{in} = 0$   $\Omega$  (because of the virtual ground at the input).  $R_o = \infty$   $\Omega$  (because  $i_L$  is independent of the value of  $R_L$ ).

(c) If  $i_I$  is in the direction shown in the figure above, the maximum allowable value of  $i_I$  will be determined by  $v_O$  reaching  $-12$  V, at which point

$$v_x = -i_{I\max} \times 10$$

and

$$v_O = -12 = v_x - i_{L\max} \times 1 = -10 i_{I\max} - 11 i_{I\max}$$

$$\Rightarrow i_{I\max} = \frac{12}{21} = 0.57 \text{ mA}$$

If  $i_I$  is in a direction opposite to that shown in the figure, then

$$v_x = 10i_I$$

$$v_O = v_x + i_L R_L = 10i_I + 11i_I = 21i_I$$

The maximum value of  $i_I$  will result in  $v_O = +12$  V. Thus

$$12 = 21i_{I\max} \Rightarrow i_{I\max} = \frac{12}{21} = 0.57 \text{ mA}$$


Thus, the allowable range of  $i_I$  is

$$-0.57 \text{ mA} \leq i_I \leq +0.57 \text{ mA}$$

(d) Since  $R_{in} = 0$ , the value of the source resistance will have no effect on the resulting  $i_L$ ,

$$i_L = 0.2 \times 11 = 2.2 \text{ mA}$$

**9.2** For the PMOS differential amplifier shown in Fig. P9.2 let  $V_{tp} = -0.8$  V and  $k'_p W/L = 4$  mA/V<sup>2</sup>. Neglect channel-length modulation.

 

**Figure P9.2**

- (a) For  $v_{G1} = v_{G2} = 0$  V, find  $|V_{OV}|$  and  $V_{SG}$  for each of  $Q_1$  and  $Q_2$ . Also find  $V_S$ ,  $V_{D1}$ , and  $V_{D2}$ .
- (b) If the current source requires a minimum voltage of 0.4 V, find the input common-mode range.

(a) For  $v_{G1} = v_{G2} = 0$  V,

$$I_{D1} = I_{D2} = \frac{1}{2} \times 0.5 = 0.25 \text{ mA}$$

$$I_{D1,2} = \frac{1}{2} k'_p \left( \frac{W}{L} \right) |V_{OV}|^2$$

$$0.25 = \frac{1}{2} \times 4 \times |V_{OV}|^2$$

$$\Rightarrow |V_{OV}| = 0.35 \text{ V}$$

$$V_{SG} = |V_{tp}| + |V_{OV}|$$

$$= 0.8 + 0.35 = 1.15 \text{ V}$$

$$V_S = 0 + V_{SG} = +1.15 \text{ V}$$

$$V_{D1} = V_{D2} = -V_{SS} + I_D R_D$$

$$= -2.5 + 0.25 \times 4$$

$$= -1.5 \text{ V}$$

Since for each of  $Q_1$  and  $Q_2$ ,

$$V_{SD} = 1.15 - (-1.5)$$

$$= 2.65 \text{ V}$$

which is greater than  $|V_{OV}|$ ,  $Q_1$  and  $Q_2$  are operating in saturation as implicitly assumed.

(b) The highest value of  $V_{CM}$  is limited by the need to keep a minimum of 0.4 V across the current source, thus

$$V_{CM\max} = +2.5 - 0.4 - V_{SG}$$

$$= +2.5 - 0.4 - 1.15 = +0.95 \text{ V}$$

The lowest value of  $V_{CM}$  is limited by the need to keep  $Q_1$  and  $Q_2$  in saturation, thus


$$V_{CM\min} = V_{D1,2} - |V_{tp}|$$

$$= -1.5 - 0.8 = -2.3 \text{ V}$$

Thus,

$$-2.3 \text{ V} \leq V_{ICM} \leq +0.95 \text{ V}$$

**D 9.6** Design the circuit in Fig. P9.6 to obtain a dc voltage of  $+0.1\text{ V}$  at each of the drains of  $Q_1$  and  $Q_2$  when  $v_{G1} = v_{G2} = 0\text{ V}$ . Operate all transistors at  $V_{OV} = 0.15\text{ V}$

 

**Figure P9.6**

and assume that for the process technology in which the circuit is fabricated,  $V_m = 0.4\text{ V}$  and  $\mu_n C_{ox} = 400\text{ }\mu\text{A/V}^2$ . Neglect channel-length modulation. Determine the values of  $R$ ,  $R_D$ , and the  $W/L$  ratios of  $Q_1$ ,  $Q_2$ ,  $Q_3$ , and  $Q_4$ . What is the input common-mode voltage range for your design?

For  $v_{G1} = v_{G2} = 0\text{ V}$ ,

$$I_{D1} = I_{D2} = \frac{0.4}{2} = 0.2\text{ mA}$$

To obtain

$$V_{D1} = V_{D2} = +0.1\text{ V}$$

$$V_{DD} - I_{D1,2} R_D = 0.1$$

$$0.9 - 0.2 R_D = 0.1$$

$$\Rightarrow R_D = 4\text{ k}\Omega$$

For  $Q_1$  and  $Q_2$ ,

$$I_{D1,2} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_{1,2} V_{OV}^2$$

$$0.2 = \frac{1}{2} \times 0.4 \left( \frac{W}{L} \right)_{1,2} \times 0.15^2$$

$$\Rightarrow \left( \frac{W}{L} \right)_{1,2} = 44.4$$

For  $Q_3$ ,

$$0.4 = \frac{1}{2} \times 0.4 \times \left( \frac{W}{L} \right)_3 \times 0.15^2$$

$$\Rightarrow \left( \frac{W}{L} \right)_3 = 88.8$$

Since  $Q_3$  and  $Q_4$  form a current mirror with  $I_{D3} = 4I_{D4}$ ,

$$\left( \frac{W}{L} \right)_4 = \frac{1}{4} \left( \frac{W}{L} \right)_3 = 22.2$$

$$V_{GS4} = V_{GS3} = V_m + V_{OV} = 0.4 + 0.15 = 0.55\text{ V}$$

$$R = \frac{0.9 - (-0.9) - 0.55}{0.1}$$

$$= 12.5\text{ k}\Omega$$

The lower limit on  $V_{CM}$  is determined by the need to keep  $Q_3$  operating in saturation. For this to happen, the minimum value of  $V_{DS3}$  is  $V_{OV} = 0.15\text{ V}$ . Thus,

$$V_{ICM\min} = -V_{SS} + V_{OV3} + V_{GS1,2}$$

$$= -0.9 + 0.15 + 0.4 + 0.15$$

$$= -0.2\text{ V}$$

The upper limit on  $V_{CM}$  is determined by the need to keep  $Q_1$  and  $Q_2$  in saturation, thus


$$V_{ICM\max} = V_{D1,2} + V_m$$

$$= 0.1 + 0.4 = 0.5\text{ V}$$

Thus,


$$-0.2\text{ V} \leq V_{ICM} \leq +0.5\text{ V}$$

**D 9.19** Figure P9.19 shows a MOS differential amplifier with the drain resistors  $R_D$  implemented using diode-connected PMOS transistors,  $Q_3$  and  $Q_4$ . Let  $Q_1$  and  $Q_2$  be matched, and  $Q_3$  and  $Q_4$  be matched.

 

**Figure P9.19**

- Find the differential half-circuit and use it to derive an expression for  $A_d$  in terms of  $g_{m1,2}$ ,  $g_{m3,4}$ ,  $r_{o1,2}$ , and  $r_{o3,4}$ .
- Neglecting the effect of the output resistances  $r_o$ , find  $A_d$  in terms of  $\mu_n$ ,  $\mu_p$ ,  $(W/L)_{1,2}$  and  $(W/L)_{3,4}$ .
- If  $\mu_n = 4\mu_p$  and all four transistors have the same channel length, find  $(W_{1,2}/W_{3,4})$  that results in  $A_d = 10$  V/V.

 

- The figure shows the differential half-circuit. Recalling that the incremental (small-signal) resistance of a diode-connected transistor is given by  $\left(\frac{1}{g_m} \parallel r_o\right)$ , the equivalent load resistance of  $Q_1$  will be

$$R_D = \frac{1}{g_{m3}} \parallel r_{o3}$$

- and the differential gain of the amplifier in Fig. P8.17 will be

$$A_d \equiv \frac{v_{od}}{v_{id}} = g_{m1} \left[ \frac{1}{g_{m3}} \parallel r_{o3} \parallel r_{o1} \right]$$

- Since both sides of the amplifier are matched, this expression can be written in a more general way as

$$A_d = g_{m1,2} \left[ \frac{1}{g_{m3,4}} \parallel r_{o3,4} \parallel r_{o1,2} \right]$$

- Neglecting  $r_{o1,2}$  and  $r_{o3,4}$  (much larger than  $1/g_{m3,4}$ ),

$$\begin{aligned} A_d &\simeq \frac{g_{m1,2}}{g_{m3,4}} \\ &= \frac{\sqrt{2\mu_n C_{ox} (W/L)_{1,2} (I/2)}}{\sqrt{2\mu_p C_{ox} (W/L)_{3,4} (I/2)}} \\ &= \sqrt{\frac{\mu_n (W/L)_{1,2}}{\mu_p (W/L)_{3,4}}} \end{aligned}$$

- $\mu_n = 4\mu_p$  and all channel lengths are equal,

$$A_d = 2 \sqrt{\frac{W_{1,2}}{W_{3,4}}}$$

- For  $A_d = 10$ ,

$$10 = 2 \sqrt{\frac{W_{1,2}}{W_{3,4}}}$$


$$\Rightarrow \frac{W_{1,2}}{W_{3,4}} = 25$$




- (a) With  $v_{G1} = v_{G2} = 0$  V, and assuming that  $Q_1$  and  $Q_2$  are operating in saturation, what dc voltages appear at the sources of  $Q_1$  and  $Q_2$ ? Express these in terms of the overdrive voltage  $V_{OV}$  at which each of  $Q_1$  and  $Q_2$  operates, and  $V_t$ .
- (b) For the situation in (a), what current flows in  $Q_3$ ? What overdrive voltage  $V_{OV3}$  is  $Q_3$  operating at, in terms of  $V_C$ ,  $V_{OV}$ , and  $V_t$ ?
- (c) Now consider the case  $v_{G1} = +v_{id}/2$  and  $v_{G2} = -v_{id}/2$ , where  $v_{id}$  is a small signal. Convince yourself that  $Q_3$  now conducts current and operates in the triode region with a small  $v_{DS}$ . What resistance  $r_{DS}$  does it have, expressed in terms of the overdrive voltage  $V_{OV3}$  at which it is operating? This is the resistance  $R_s$ . Now if all three transistors have the same  $W/L$ , express  $R_s$  in terms of  $V_{OV}$ ,  $V_{OV3}$ , and  $g_{m1,2}$ .
- (d) Find  $V_{OV3}$  and hence  $V_C$  that result in (i)  $R_s = 1/g_{m1,2}$ ; (ii)  $R_s = 0.5/g_{m1,2}$ .

$$v_{GS1} = v_{GS2} = V_{OV1,2} + V_{tn}$$
$$\Rightarrow V_C = V_{OV1,2}$$

 
**9.47** For each of the emitter-degenerated differential amplifiers shown in Fig. P9.47, find the differential half-circuit and derive expressions for the differential gain  $A_d$  and differential input resistance  $R_{id}$ . For each circuit, what dc voltage appears across the bias current source(s) in the quiescent state (i.e., with  $v_{id} = 0$ )? Hence, which of the two circuits will allow a larger negative  $V_{CM}$ ?



(a)

 

(b)

 

Both circuits have the same differential half-circuit shown in the figure. Thus, for both

$$A_d = \frac{\alpha R_C}{r_e + R_e}$$

$$R_{id} = (\beta + 1)(2r_e + 2R_e)$$

$$= 2(\beta + 1)(r_e + R_e)$$

With  $v_{id} = 0$ , the dc voltage appearing at the top end of the bias current source will be

$$(a) \quad V_{CM} - V_{BE} - \left(\frac{I}{2}\right)R_C$$

$$(b) \quad V_{CM} - V_{BE}$$

Since circuit (b) results in a larger voltage across the current source and given that the minimum value of  $V_{CM}$  is limited by the need to keep a certain specified minimum voltage across the current source, we see that circuit (b) will allow a larger negative  $V_{CM}$ .

**Figure P9.47**

**SIM D \*9.57** The differential amplifier in Fig. P9.57 utilizes a resistor  $R_{SS}$  to establish a 1-mA dc bias current. Note that this amplifier uses a single 5-V supply and thus the dc common-mode voltage  $V_{CM}$  cannot be zero. Transistors  $Q_1$  and  $Q_2$  have  $k'_n W/L = 2.5 \text{ mA/V}^2$ ,  $V_t = 0.7 \text{ V}$ , and  $\lambda = 0$ .

- Find the required value of  $V_{CM}$ .
- Find the value of  $R_D$  that results in a differential gain  $A_d$  of 8 V/V.
- Determine the dc voltage at the drains.
- Determine the single-ended-output common-mode gain  $\Delta V_{D1}/\Delta V_{CM}$ . (Hint: You need to take  $1/g_m$  into account.)
- Use the common-mode gain found in (d) to determine the change in  $V_{CM}$  that results in  $Q_1$  and  $Q_2$  entering the triode region.

 


Figure P9.57

(a) Assume  $v_{id} = 0$  and the two sides of the differential amplifier are matched. Thus,

$$I_{D1} = I_{D2} = 0.5 \text{ mA}$$

$$I_{D1,2} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) V_{OV}^2$$

$$0.5 = \frac{1}{2} \times 2.5 \times V_{OV}^2$$

$$\Rightarrow V_{OV} = 0.632 \text{ V}$$

$$V_{CM} = V_{GS} + 1 \text{ mA} \times R_{SS}$$

$$= V_t + V_{OV} + 1 \times R_{SS}$$

$$= 0.7 + 0.632 + 1$$

$$= 2.332 \text{ V}$$

$$(b) \quad g_m = \frac{2I_D}{V_{OV}} = \frac{2 \times 0.5}{0.632} = 1.58 \text{ mA/V}$$

$$A_d = g_m R_D$$


$$8 = 1.38 \times R_D$$

$$\Rightarrow R_D = 5.06 \text{ k}\Omega$$

$$(c) \quad V_{D1} = V_{D2} = V_{DD} - I_D R_D$$

$$= 5 - 0.5 \times 5.06 = 2.47 \text{ V}$$

(d)

 

The figure shows the common-mode half-circuit,

$$\frac{\Delta V_{D1}}{\Delta V_{CM}} = - \frac{R_D}{\frac{1}{g_m} + 2 R_{SS}}$$

$$\frac{\Delta V_{D1}}{\Delta V_{CM}} = - \frac{5.06}{\frac{1}{1.58} + 2} = -1.92 \text{ V/V}$$

(e) For  $Q_1$  and  $Q_2$  to enter the triode region

$$V_{CM} + \Delta V_{CM} = V_t + V_{D1} + \Delta V_{D1}$$

Substituting  $V_{CM} = 2.332$ ,  $V_t = 0.7 \text{ V}$ ,  $V_{D1} = 2.47 \text{ V}$ , and  $\Delta V_{D1} = -1.92 \Delta V_{CM}$  results in


$$2.332 + \Delta V_{CM} = 0.7 + 2.47 - 1.92 \Delta V_{CM}$$

$$\Rightarrow \Delta V_{CM} = 0.287 \text{ V}$$

With this change,  $V_{CM} = 2.619 \text{ V}$  and  $V_{D1,2} = 1.919 \text{ V}$ ; thus  $V_{CM} = V_t + V_{D1,2}$ .



**9.81** One approach to “offset correction” involves the adjustment of the values of  $R_{C1}$  and  $R_{C2}$  so as to reduce the differential output voltage to zero when both input terminals are grounded. This offset-nulling process can be accomplished by utilizing a potentiometer in the collector circuit, as shown in Fig. P9.81. We wish to find the

 

**Figure P9.81**

potentiometer setting, represented by the fraction  $x$  of its value connected in series with  $R_{C1}$ , that is required for nulling the output offset voltage that results from:

- (a)  $R_{C1}$  being 4% higher than nominal and  $R_{C2}$  4% lower than nominal
- (b)  $Q_1$  having an area 5% larger than nominal, while  $Q_2$  has area 5% smaller than nominal.

(a)  $R_{C1} = 1.04 \times 5 = 5.20 \text{ k}\Omega$

$R_{C2} = 0.96 \times 5 = 4.80 \text{ k}\Omega$

To equalize the total resistance in each collector, we adjust the potentiometer so that

$$R_{C1} + x \times 1 \text{ k}\Omega = R_{C2} + (1 - x) \times 1 \text{ k}\Omega$$

$$5.2 + x = 4.8 + 1 - x$$

$$\Rightarrow x = 0.3 \text{ k}\Omega$$

(b) If the area of  $Q_1$  and hence  $I_{S1}$  is 5% larger than nominal, then we have

$$I_{S1} = 1.05I_S$$

and the area of  $Q_2$  and hence  $I_{S2}$  is 5% smaller than nominal,

$$I_{S2} = 0.95I_S$$

Thus,

$$I_{E1} = 0.5 \times 1.05 = 0.525 \text{ mA}$$

$$I_{E2} = 0.5 \times 0.95 = 0.475 \text{ mA}$$

Assuming  $\alpha \simeq 1$ , we obtain

$$I_{C1} = 0.525 \text{ mA} \quad I_{C2} = 0.475 \text{ mA}$$

To reduce the resulting offset to zero, we adjust the potentiometer so that

$$V_{C1} = V_{C2}$$

$$\Rightarrow V_{CC} - (R_{C1} + x)I_{C1} = V_{CC} - (R_{C2} + 1 - x)I_{C2}$$

$$I_{C1}(R_{C1} + x) = I_{C2}(R_{C2} + 1 - x)$$

$$0.525(5 + x) = 0.475(5 + 1 - x)$$

$$\Rightarrow x = 0.225$$

**D 10.5** The amplifier in Fig. P10.5 is biased to operate at  $g_m = 2 \text{ mA/V}$ . Neglect  $r_o$ .

 


Figure P10.5

- Determine the value of  $R_D$  that results in a midband gain of  $-20 \text{ V/V}$ .
- Determine the value of  $C_S$  that results in a pole frequency of  $100 \text{ Hz}$ .
- What is the frequency of the transmission zero introduced by  $C_S$ ?
- Give an approximate value for the 3-dB frequency  $f_L$ .
- Sketch a Bode plot for the gain of this amplifier. What does the plot tell you about the gain at dc? Does this make sense? Why or why not?

(e) The Bode plot for the gain is shown in Fig. 2.

 


Figure 2

Observe that the dc gain is  $6 \text{ dB}$ , i.e.  $2 \text{ V/V}$ . This makes perfect sense since from Fig. 1 we see that at dc, capacitor  $C_S$  behaves as open circuit and the gain becomes

$$\begin{aligned} \text{DC gain} &= -\frac{R_D}{\frac{1}{g_m} + R_S} = -\frac{10 \text{ k}\Omega}{\left(\frac{1}{2} + 4.5\right)} \\ &= -2 \text{ V/V} \end{aligned}$$

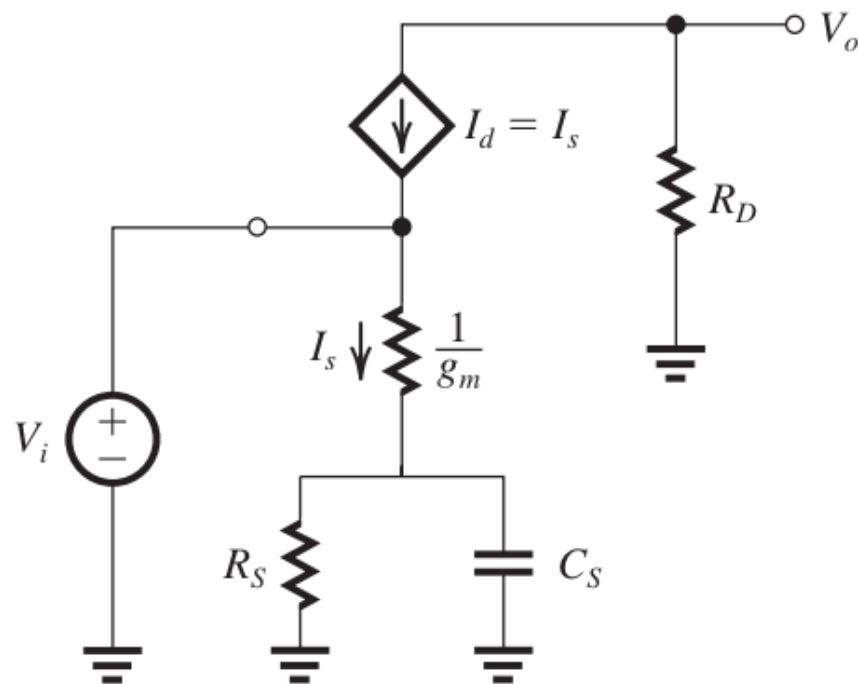


Figure 1

Replacing the MOSFET with its  $T$  model results in the circuit shown in Fig. 1.

$$(a) A_M \equiv \frac{V_o}{V_i} = -g_m R_D$$

$$-20 = -2 \times R_D$$

$$\Rightarrow R_D = 10 \text{ k}\Omega$$

$$(b) f_P = \frac{g_m + 1/R_S}{2\pi C_S}$$

$$100 = \frac{2 \times 10^{-3} + (1/4.5 \times 10^3)}{2\pi C_S}$$

$$\Rightarrow C_S = 3.53 \text{ }\mu\text{F}$$

$$(c) f_Z = \frac{1}{2\pi C_S R_S} =$$

$$\frac{1}{2\pi \times 3.53 \times 10^{-6} \times 4.5 \times 10^3} = 10 \text{ Hz}$$

$$(d) \text{ Since } f_P \gg f_Z,$$

$$f_L \simeq f_P = 100 \text{ Hz}$$

**10.15** Starting from the expression of  $f_T$  for a MOSFET,

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

and making the approximation that  $C_{gs} \gg C_{gd}$  and that the overlap component of  $C_{gs}$  is negligibly small, show that

$$f_T \simeq \frac{1.5}{\pi L} \sqrt{\frac{\mu_n I_D}{2C_{ox} WL}}$$

Thus note that to obtain a high  $f_T$  from a given device, it must be operated at a high current. Also note that faster operation is obtained from smaller devices.

$$\mathbf{9.15} \quad f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

For  $C_{gs} \gg C_{gd}$

$$f_T \simeq \frac{g_m}{2\pi C_{gs}} \quad (1)$$

$$C_{gs} = \frac{2}{3} WLC_{ox} + WL_{ov}C_{ox}$$

If the overlap component ( $WL_{ov}C_{ox}$ ) is small, we get

$$C_{gs} \simeq \frac{2}{3} WLC_{ox} \quad (2)$$

The transconductance  $g_m$  is given by

$$g_m = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right) I_D} \quad (3)$$

Substituting from (2) and (3) into (1), we get

$$\begin{aligned} f_T &= \frac{\sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right) I_D}}{2\pi \times \frac{2}{3} WLC_{ox}} \\ &= \frac{1.5}{\pi L} \sqrt{\frac{\mu_n I_D}{2C_{ox} WL}} \quad \text{Q.E.D.} \end{aligned}$$

We observe that for a given device,  $f_T$  is proportional to  $\sqrt{I_D}$ ; thus to obtain faster operation the MOSFET is operated at a higher  $I_D$ .

Also, we observe that  $f_T$  is inversely proportional to  $L\sqrt{WL}$ ; thus faster operation is obtained from smaller devices.

**10.20** An *npn* transistor is operated at  $I_C = 1$  mA and  $V_{CB} = 2$  V. It has  $\beta_0 = 100$ ,  $V_A = 50$  V,  $\tau_F = 30$  ps,  $C_{je0} = 20$  fF,  $C_{\mu0} = 30$  fF,  $V_{0c} = 0.75$  V,  $m_{CBJ} = 0.5$ , and  $r_x = 100$   $\Omega$ . Sketch the complete hybrid- $\pi$  model, and specify the values of all its components. Also, find  $f_T$ .

**9.19**  $r_x = 100$   $\Omega$

$$g_m = \frac{I_C}{V_T} = \frac{1 \text{ mA}}{0.025 \text{ V}} = 40 \text{ mA/V}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{40} = 2.5 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_C} = \frac{50}{1} = 50 \text{ k}\Omega$$

$$C_{de} = \tau_F g_m = 30 \times 10^{-12} \times 40 \times 10^{-3} = 1.2 \text{ pF}$$

$$C_{je0} = 20 \text{ pF}$$

$$C_\pi = C_{de} + 2C_{je0} = 1.2 + 2 \times 0.02 = 1.24 \text{ pF}$$

$$C_\mu = \frac{C_{je0}}{\left(1 + \frac{V_{CB}}{V_{0c}}\right)^m}$$

$$C_\mu = \frac{20}{\left(1 + \frac{2}{0.75}\right)^{0.5}} = 10.4 \text{ fF}$$

$$* C_\mu = \frac{30}{\left(1 + \frac{2}{0.75}\right)^{0.5}}$$


$$f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)}$$

$$= \frac{40 \times 10^{-3}}{2\pi(1.24 + 0.01) \times 10^{-12}}$$

$$= 5.1 \text{ GHz} \quad 5.07 \text{ GHz}$$

$$= 15.667 \text{ fF}$$

This figure belongs to Problem 9.18.

 

**10.32** A discrete MOSFET common-source amplifier has  $R_G = 2 \text{ M}\Omega$ ,  $g_m = 5 \text{ mA/V}$ ,  $r_o = 100 \text{ k}\Omega$ ,  $R_D = 20 \text{ k}\Omega$ ,  $C_{gs} = 3 \text{ pF}$ , and  $C_{gd} = 0.5 \text{ pF}$ . The amplifier is fed from a voltage source with an internal resistance of  $500 \text{ k}\Omega$  and is connected to a  $20\text{-k}\Omega$  load. Find:

- (a) the overall midband gain  $A_M$
- (b) the upper 3-dB frequency  $f_H$
- (c) the frequency of the transmission zero,  $f_Z$ .

$$\mathbf{9.29} \quad (\text{a}) \quad A_M = -\frac{R_G}{R_G + R_{\text{sig}}} g_m R'_L$$

where

$$\begin{aligned} R'_L &= R_D \parallel R_L \parallel r_o \\ &= 20 \text{ k}\Omega \parallel 20 \text{ k}\Omega \parallel 100 \text{ k}\Omega \\ &= 9.1 \text{ k}\Omega \end{aligned}$$

$$\begin{aligned} A_M &= -\frac{2 \text{ M}\Omega}{2 \text{ M}\Omega + 0.5 \text{ M}\Omega} \times 5 \times 9.1 \\ &= -36.4 \text{ V/V} \end{aligned}$$

$$(\text{b}) \quad f_H = \frac{1}{2\pi C_{\text{in}} R'_{\text{sig}}}$$

where

$$\begin{aligned} C_{\text{in}} &= C_{gs} + C_{gd}(1 + g_m R'_L) \\ &= 3 + 0.5(1 + 5 \times 9.1) \\ &= 26.25 \text{ pF} \end{aligned}$$

and

$$\begin{aligned} R'_{\text{sig}} &= R_{\text{sig}} \parallel R_G \\ &= 500 \text{ k}\Omega \parallel 2000 \text{ k}\Omega \\ &= 400 \text{ k}\Omega \end{aligned}$$

Thus,

$$\begin{aligned} f_H &= \frac{1}{2\pi \times 26.25 \times 10^{-12} \times 400 \times 10^3} \\ &= 15.2 \text{ kHz} \end{aligned}$$

$$\begin{aligned} (\text{c}) \quad f_Z &= \frac{g_m}{2\pi C_{gd}} \\ &= \frac{5 \times 10^{-3}}{2\pi \times 0.5 \times 10^{-12}} \\ &= 1.6 \text{ GHz} \end{aligned}$$



**10.52** An amplifier with a dc gain of 60 dB has a single-pole, high-frequency response with a 3-dB frequency of 100 kHz.

- Give an expression for the gain function  $A(s)$ .
- Sketch Bode diagrams for the gain magnitude and phase.
- What is the gain–bandwidth product?
- What is the unity-gain frequency?
- If a change in the amplifier circuit causes its transfer function to acquire another pole at 1 MHz, sketch the resulting gain magnitude and specify the unity-gain frequency. Note that this is an example of an amplifier with a unity-gain bandwidth that is different from its gain–bandwidth product.

**9.47** (a)  $A(s) = 1000 \frac{1}{1 + s/(2\pi \times 10^5)}$

 


Figure 1

Figure 1 shows the Bode plot for the gain magnitude and phase.

(c)  $GB = 1000 \times 100 \text{ kHz} = 100 \text{ MHz}$

(d) The unity-gain frequency  $f_t$  is

$f_t = 100 \text{ MHz}$

(e)

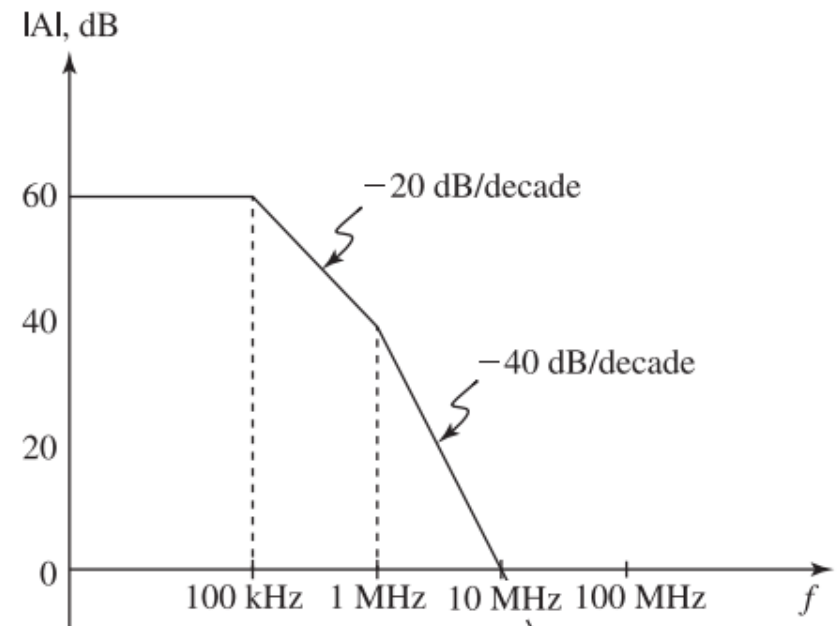


Figure 2

Figure 2 shows the magnitude response when a second pole at 1 MHz appears in the transfer function. The unity-gain frequency  $f_t$  now is

$f_t = 10 \text{ MHz}$

which is different from the gain–bandwidth product,

$GB = 100 \text{ MHz}$